

# Lesson 5

## *Digital Logic*

---

Junying Chen

# From Logic to Gates

- Two-level logic: ANDs followed by ORs
- Example:  $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$

