

Lesson 10

Digital Logic

Junying Chen

In-class Test 2 Answers

- 2.1

- Recall **SOP canonical form** (Page 59).
- **Sum** the **minterms** of all the rows (in the truth table) **with outputs as 1's**.

$$(a) Y = \bar{A}\bar{B} + A\bar{B} + AB = \sum(m_1, m_2, m_3) = \sum(1, 2, 3)$$

$$(b) Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC \\ = \sum(m_1, m_2, m_3, m_4, m_6) = \sum(1, 2, 3, 4, 6)$$

- Some students **simplified** the equation.
- **Incorrect**, because the question asks for **canonical form**.



In-class Test 2 Answers

- 2.2(a)
 - You can choose to use **Boolean theorems or K-maps**.
 - For 2-variable equations, using Boolean algebra to simplify the equations is easy. For 3- and 4-variable equations, using K-maps is more convenient. **K-maps** are usually used for equations with **up to 4 variables**.

$$\begin{aligned} Y &= \bar{A}B + A\bar{B} + AB = \bar{A}B + A\bar{B} + (AB + AB) \\ &= (\bar{A}B + AB) + (A\bar{B} + AB) = (\bar{A} + A)B + (\bar{B} + B)A \\ &= B + A = A + B \end{aligned}$$

- Some students used Boolean algebra to simplify the equation but got the result as **AB+A** or **AB+B**.
- This is **not the minimized form**.



In-class Test 2 Answers

- 2.2(a) (continued)

Use K-map:

- **Variable coding method**: Gray code (The adjacent codes have only one bit changed.)

Y A \ B		0	1
		0	1
0	0	0	1
1	0	1	1

$$Y = A + B$$

In-class Test 2 Answers

- 2.2(b)

Y C \ AB	AB			
	00	01	11	10
0	0	1	1	1
1	1	1	0	0

Solution 1:

$$Y = \overline{A}C + B\overline{C} + A\overline{C}$$

Y C \ AB	AB			
	00	01	11	10
0	0	1	1	1
1	1	1	0	0

Solution 2:


$$Y = \overline{A}C + \overline{A}B + A\overline{C}$$



In-class Test 2 Answers

- 2.3(a)


$$Y = A + B$$

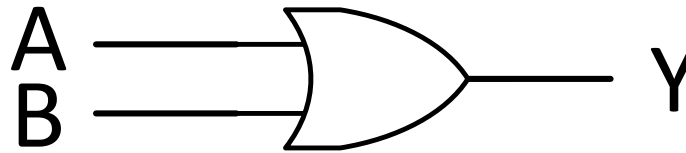


In-class Test 2 Answers

- 2.3(b)

Solution 1: $Y = \bar{A}C + B\bar{C} + A\bar{C}$

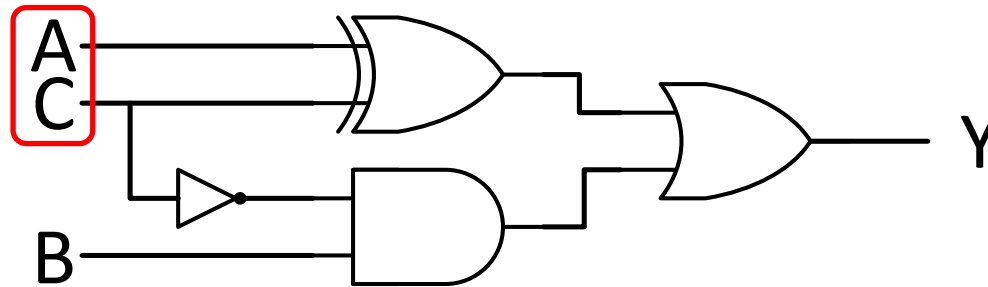

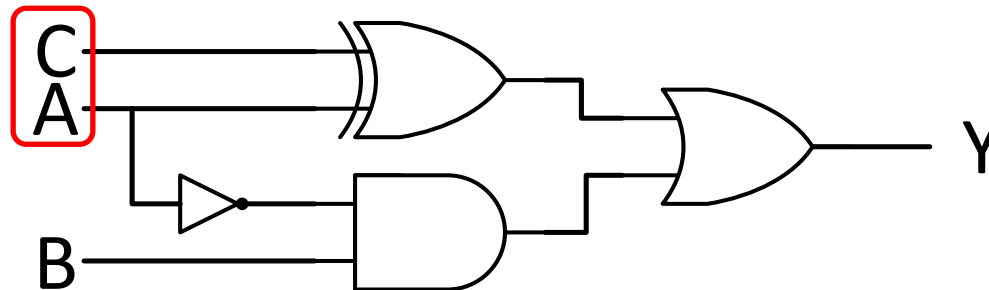Solution 2: $Y = \bar{A}C + \bar{A}B + A\bar{C}$



In-class Test 2 Answers

- 2.4
 - Need not minimize the equation.

$$Y = \bar{A}D + A\bar{C}D + A\bar{B}C + ABCD$$

$$Z = BD + A\bar{C}D$$

In-class Test 2 Answers

- 2.5

– **Minimal** Boolean equation (several solutions)

Solution 1:

Y \ AB \ CD	00	01	11	10
00	X	0	1	1
01	X	X	1	0
11	0	X	1	1
10	X	0	X	X

$$Y = BD + A\bar{D} + AC$$

Solution 2:

Y \ AB \ CD	00	01	11	10
00	X	0	1	1
01	X	X	1	0
11	0	X	1	1
10	X	0	X	X

$$Y = AB + A\bar{D} + AC$$

In-class Test 2 Answers

- 2.5 (continued)

Solution 3:

Y CD \ AB	00	01	11	10
	00	01	11	10
00	X	0	1	1
01	X	X	1	0
11	0	X	1	1
10	X	0	X	X

$$Y = AB + AC + \overline{B}\overline{D}$$

In-class Test 2 Answers

• 2.6

A3	A2	A1	A0	P	D
0	0	0	0	0	1
0	0	0	1	0	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	1	0	1

P A1A0 \ A3A2				
	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	1	1	0	1
10	1	0	0	0

P A1A0 \ A3A2				
	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	1	1	0	1
10	1	0	0	0

Solution 1:

$$P = A_2 \bar{A}_1 A_0 + \bar{A}_3 A_2 A_0 + \bar{A}_2 A_1 A_0 + \bar{A}_3 \bar{A}_2 A_1$$

Solution 2:

$$P = A_2 \bar{A}_1 A_0 + \bar{A}_3 A_1 A_0 + \bar{A}_2 A_1 A_0 + \bar{A}_3 \bar{A}_2 A_1$$

In-class Test 2 Answers

• 2.6 (continued)

A3	A2	A1	A0	P	D
0	0	0	0	0	1
0	0	0	1	0	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	1	0	1

D A1A0 \ A3A2				
	00	01	11	10
00	1	0	1	0
01	0	0	0	1
11	1	0	1	0
10	0	1	0	0


$$\begin{aligned}
 D = & A_3 A_2 \bar{A}_1 A_0 + A_3 \bar{A}_2 \bar{A}_1 A_0 \\
 & + \bar{A}_3 \bar{A}_2 A_1 A_0 + A_3 A_2 A_1 A_0 \\
 & + \bar{A}_3 A_2 A_1 \bar{A}_0 + \bar{A}_3 \bar{A}_2 \bar{A}_1 \bar{A}_0
 \end{aligned}$$

- Basically, you have to write out every bit value of the input variables in the truth table.
- But you can also write the truth table with **input don't cares**.

In-class Test 2 Answers

• 2.7

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

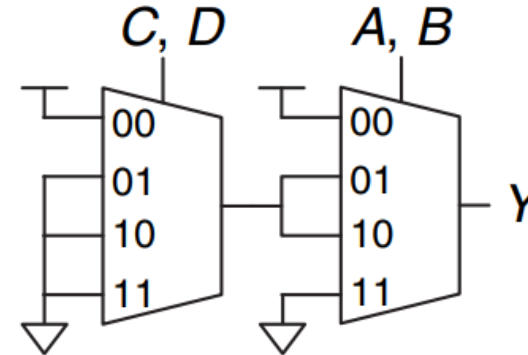


Y \ AB \ CD	00	01	11	10
00	1	1	0	1
01	1	0	0	0
11	1	0	0	0
10	1	0	0	0

$$Y = \overline{\overline{A}}\overline{\overline{B}} + \overline{\overline{A}}\overline{\overline{C}}\overline{\overline{D}} + \overline{\overline{B}}\overline{\overline{C}}\overline{\overline{D}}$$

In-class Test 2 Answers

- 2.8(a)

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

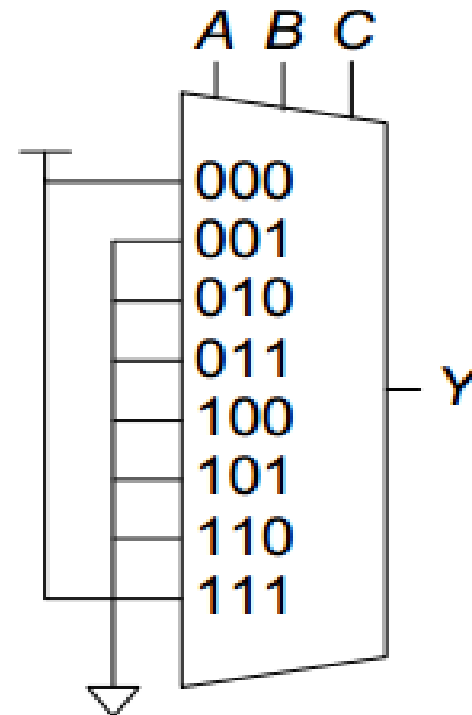


In-class Test 2 Answers

- 2.8(b)

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

A	B	Y
0	0	C'
0	1	0
1	0	0
1	1	C

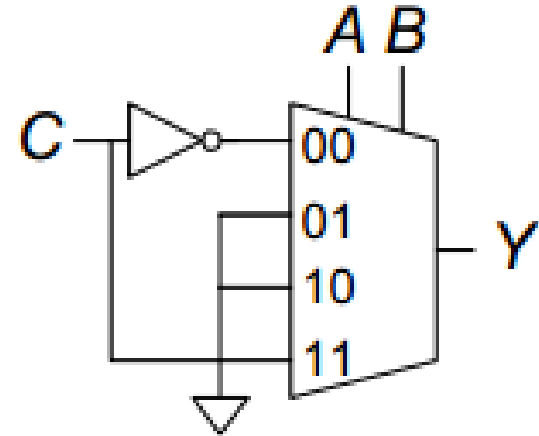

In-class Test 2 Answers


- 2.8(c)

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


A	Y
0	$B'C'$
1	BC

Solution 2:

$$\overline{BC} = \overline{B + C}$$

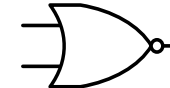

Solution 1:

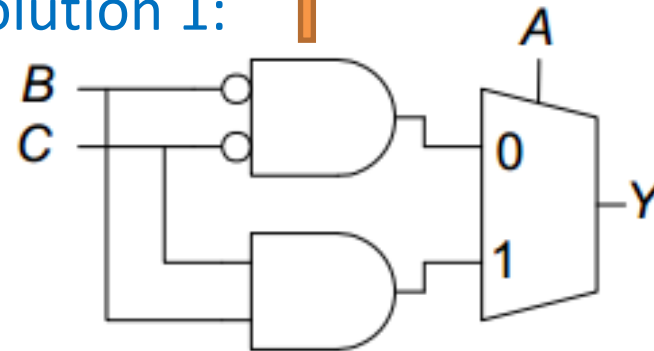

In-class Test 2 Answers

- 2.8(c) (continued)

Solution 3:

- From truth table, we learn that when **A, B and C are of the same value, Y outputs 1.**


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$A \oplus B$	Y
0	0
1	$A \oplus C$

\downarrow

$\overline{B \oplus C}$

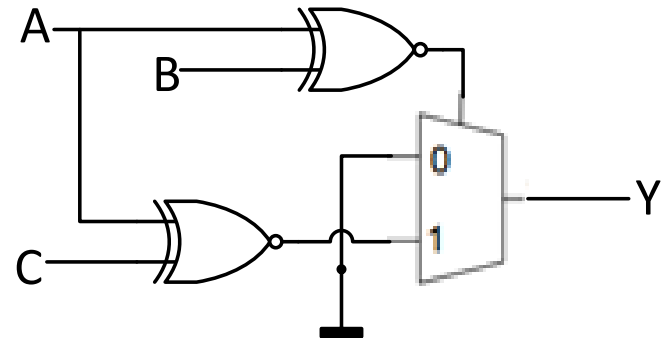A and B are interchangeable for this term.



In-class Test 2 Answers

- 2.8(c) (continued)


Solution 4:

- From truth table, we learn that when **A, B and C are of the same value, Y outputs 1.**

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


A and B are interchangeable for this term.

$A \oplus B$	Y
0	$A \oplus C$
1	0

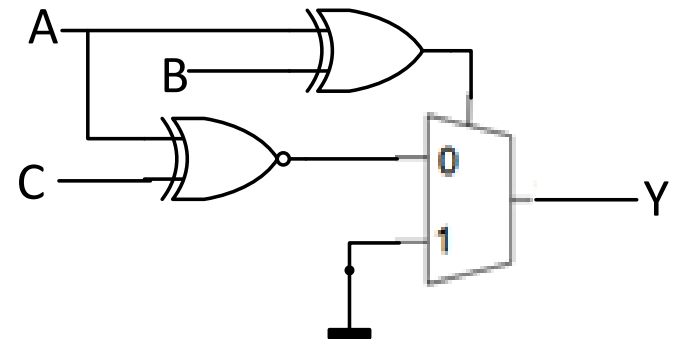

In-class Test 2 Answers

• 2.9

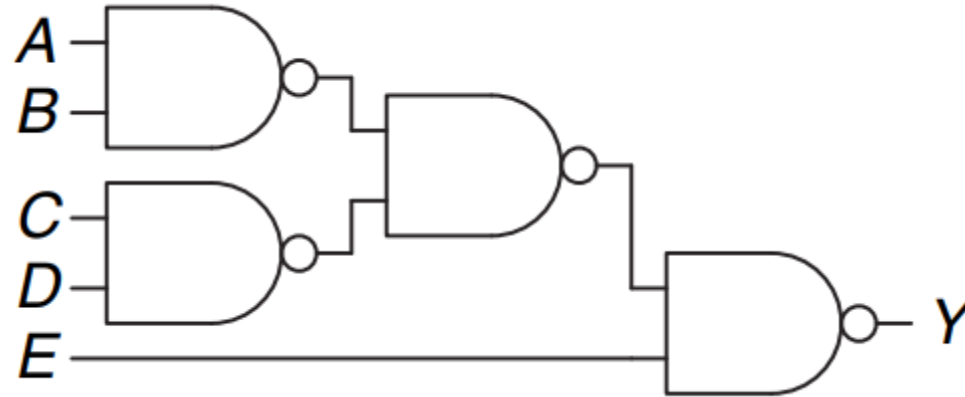

- Longest path: from A/B/C/D to Y
- Shortest path: from E to Y

$$t_{pd} = t_{pd_AY} = 3t_{pd_NAND2} = 3 \times 20 = 60\text{ps}$$

$$t_{cd} = t_{cd_EY} = t_{cd_NAND2} = 15\text{ps}$$