

## Lesson 6

# *Digital Logic*


---

Junying Chen

# From Logic to Gates

- Two-level logic: ANDs followed by ORs
- Example:  $Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C}$

$A, B, C$

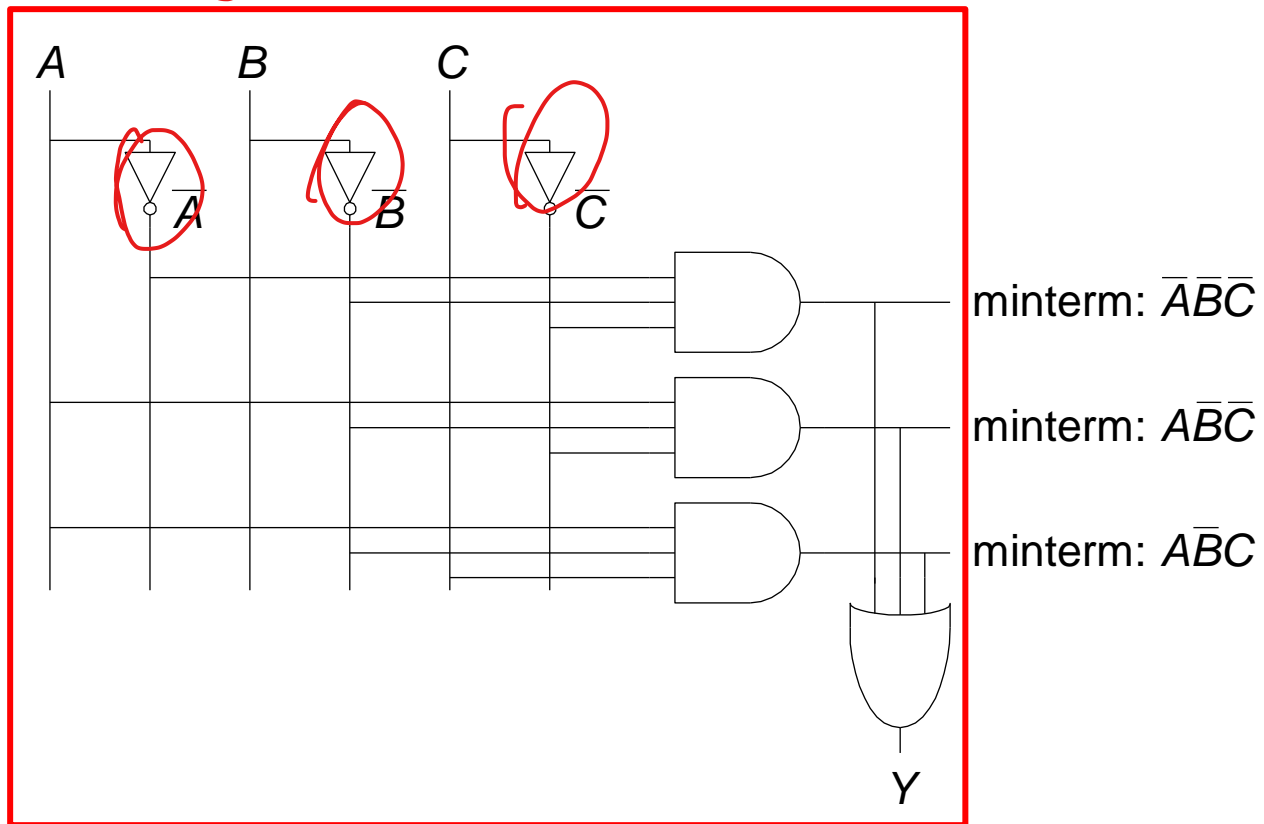


# Circuit Schematics Rules

- Inputs on the left (or top)
- Outputs on right (or bottom)
- Gates flow from left to right
- Straight wires are best


# Circuit Schematic Rules (cont.)

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect  
at a T junction

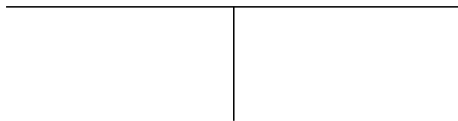

wires connect  
at a dot

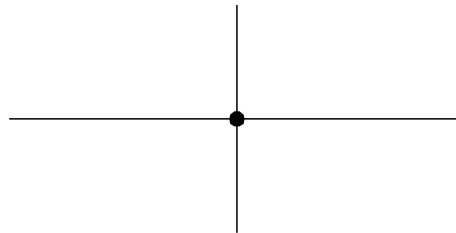

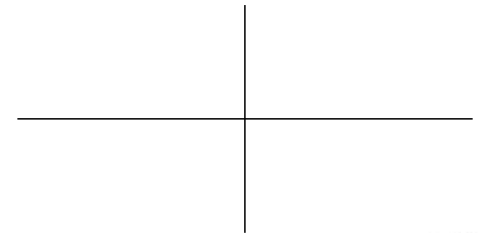
wires crossing  
without a dot do  
not connect



# Multiple-Output Circuits

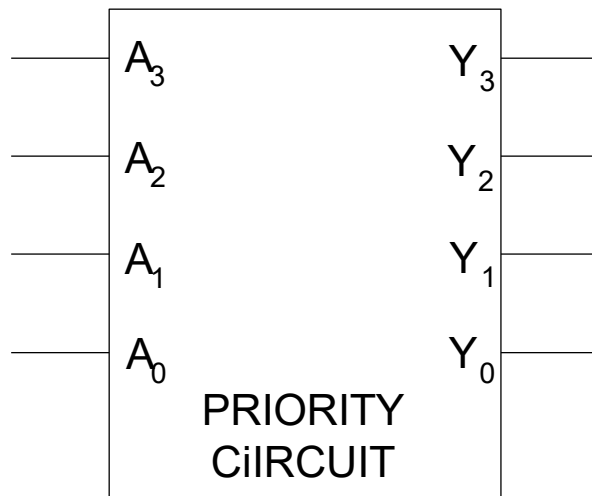- Example: Priority Circuit**

Output asserted  
corresponding to  
most significant  
TRUE input




$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0				
0	0	0	1				1
0	0	1	0			1	
0	0	1	1			1	
0	1	0	0		1		
0	1	0	1		1		
0	1	1	0		1		
0	1	1	1		1		
1	0	0	0	1			
1	0	0	1	1			
1	0	1	0	1			
1	0	1	1	1			
1	1	0	0	1			
1	1	0	1	1			
1	1	1	0	1			
1	1	1	1	1			
1	1	1	1	1			

# Multiple-Output Circuits

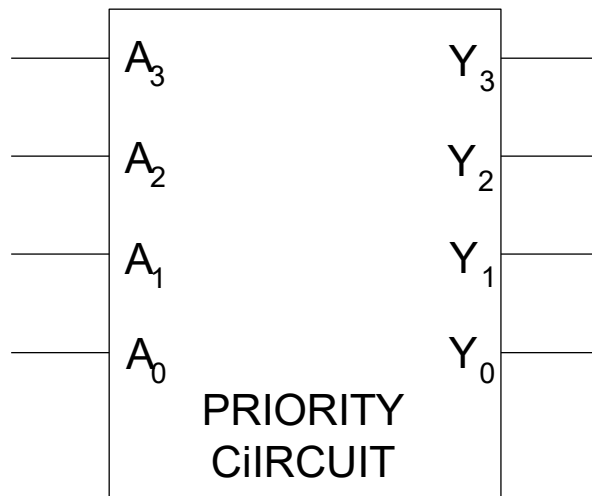- Example: Priority Circuit**


Output asserted  
corresponding to  
most significant  
TRUE input



$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0

# Priority Circuit Hardware

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

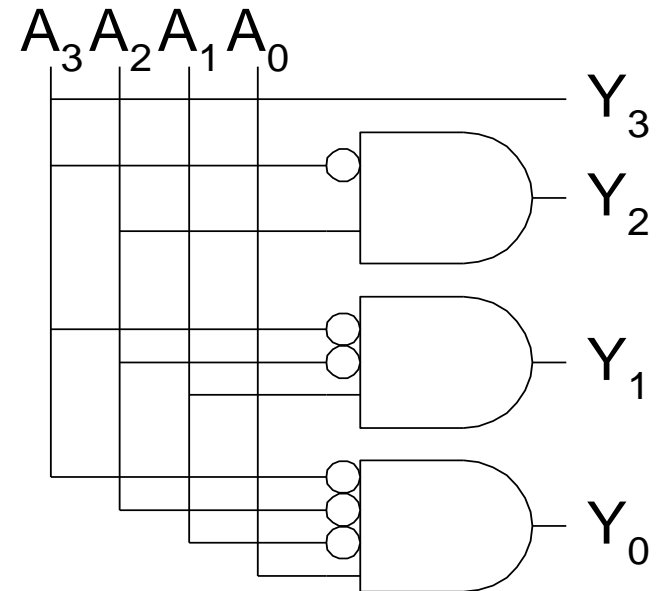

$$Y_3 = A_3$$

$$Y_2 = \bar{A}_3 A_2$$

$$Y_1 = \bar{A}_3 \bar{A}_2 A_1$$

$$Y_0 = \bar{A}_3 \bar{A}_2 \bar{A}_1 A_0$$

# Don't Cares



$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

$A_3$	$A_2$	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0




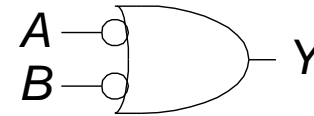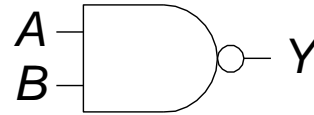
# De Morgan's Theorem

- $Y = \overline{AB} = \overline{A} + \overline{B}$



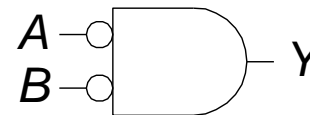
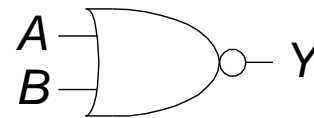
- $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$



# Bubble Pushing



- **Backward:**

- Body changes
- Adds bubbles to inputs

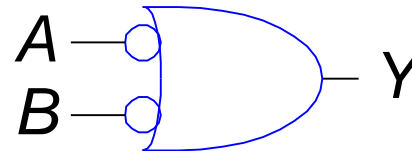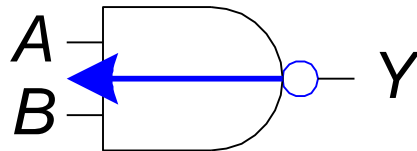


- **Forward:**

- Body changes
- Adds bubble to output

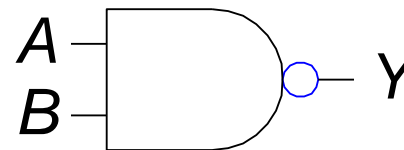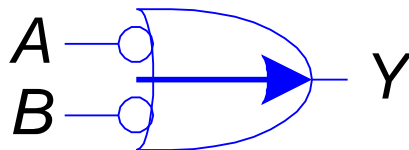

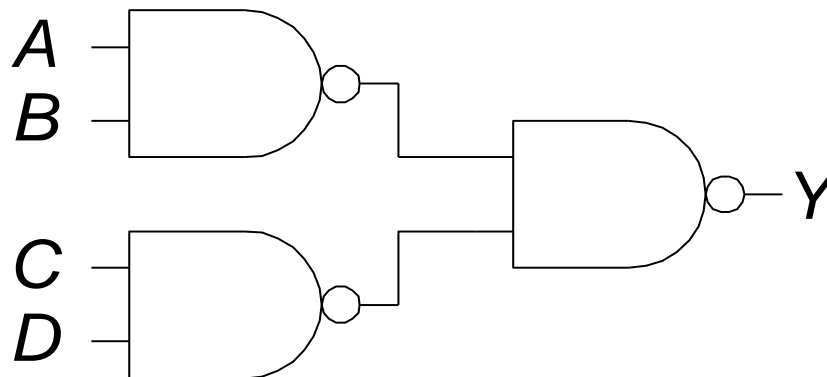
# Bubble Pushing

- What is the Boolean expression for this circuit?


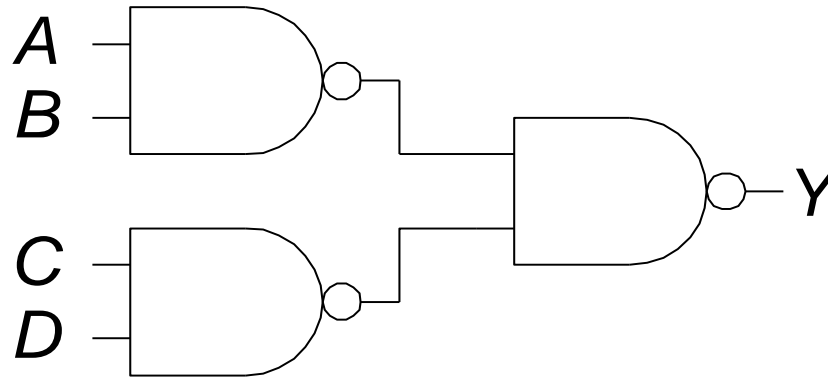
# Bubble Pushing


- What is the Boolean expression for this circuit?



$$Y = \overline{\overline{AB}} \overline{\overline{CD}} = \overline{\overline{AB}} + \overline{\overline{CD}} = AB + CD$$

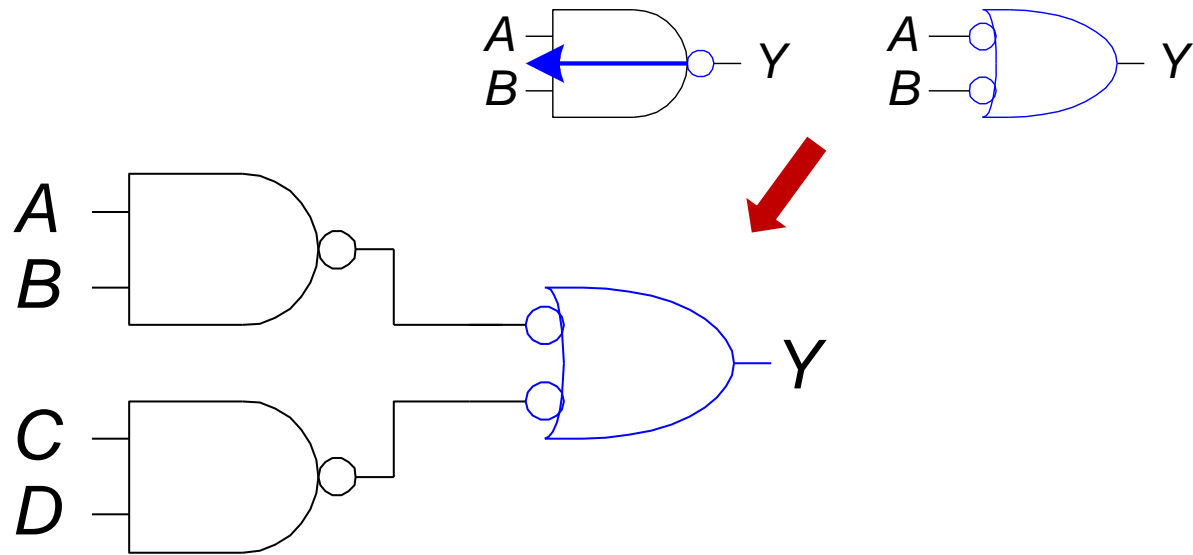
# Bubble Pushing

- What is the Boolean expression for this circuit?


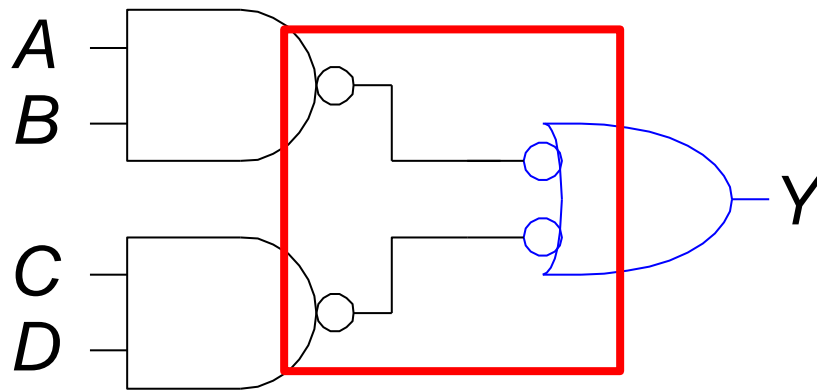
# Bubble Pushing


- What is the Boolean expression for this circuit?




$$Y = AB + CD$$
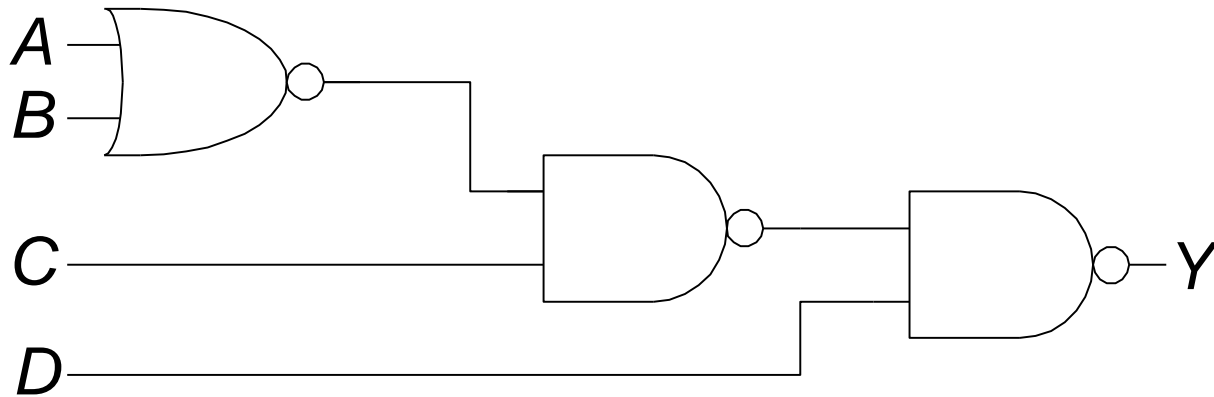
# Bubble Pushing Rules

- Begin at output, then work towards inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel





# Bubble Pushing Example


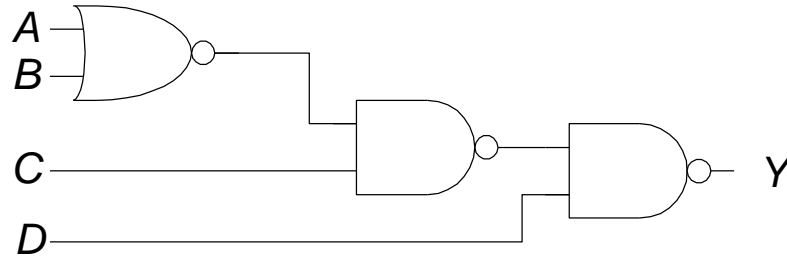







# Bubble Pushing Example

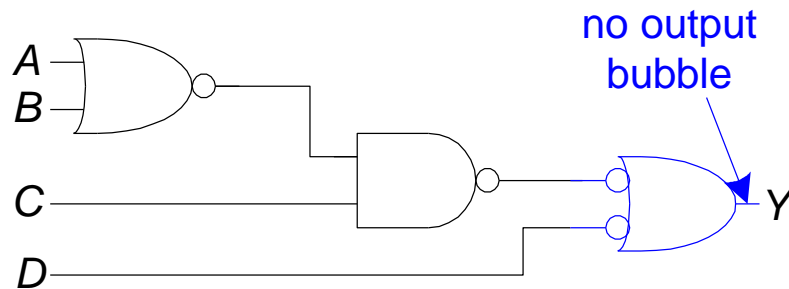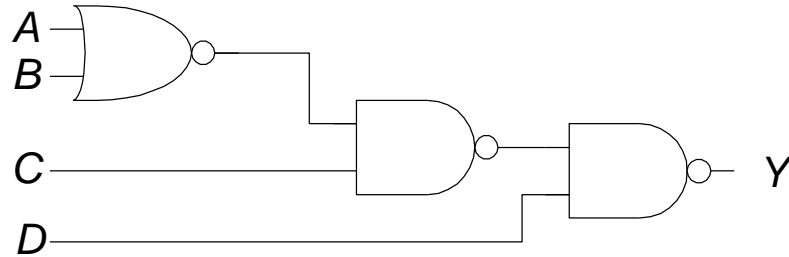

# Bubble Pushing Example

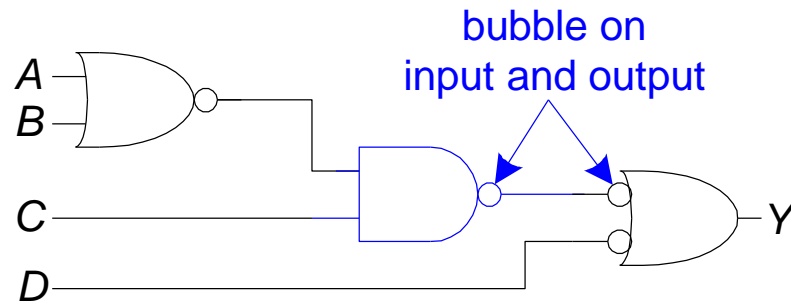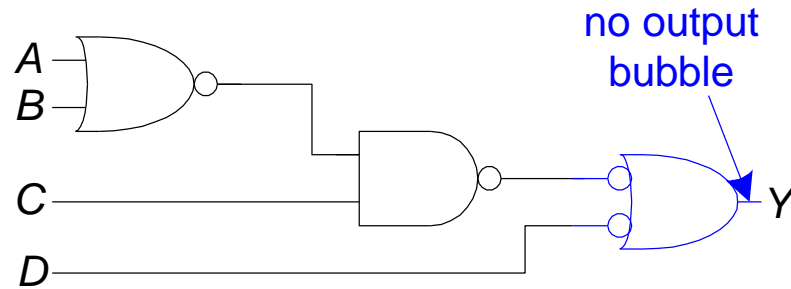


# Bubble Pushing Example

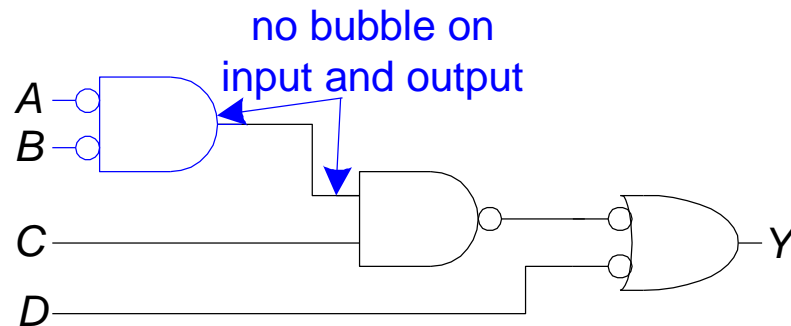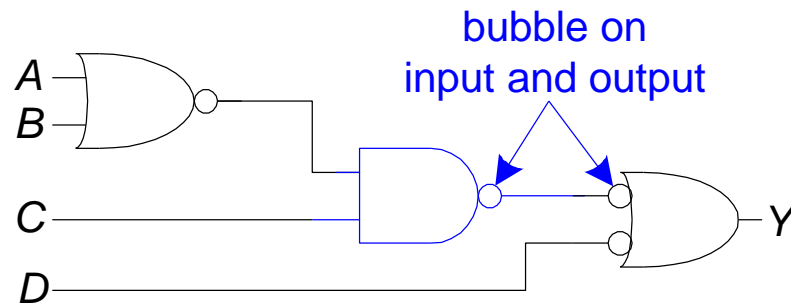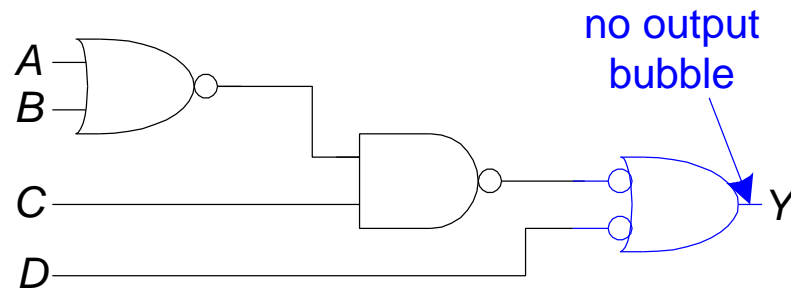

$$Y = \overline{A}\overline{B}C + \overline{D}$$
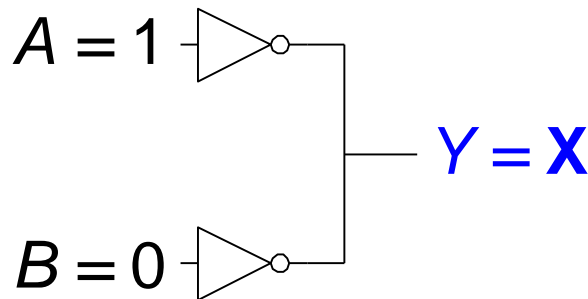
# Contention: X

- Contention: circuit tries to drive output to 1 **and** 0
  - Actual value somewhere in between
  - Could be 0, 1, or in forbidden zone
  - Might change with voltage, temperature, time, noise
  - Often causes excessive power dissipation




- **Warnings:**
  - Contention usually indicates a **bug**.
  - **X** is used for “don’t care” and contention - look at the context to tell them apart

# Floating: Z

- Floating, high impedance, open, high Z
- Floating output might be 0, 1, or somewhere in between
  - A voltmeter won't indicate whether a node is floating


## Tristate Buffer

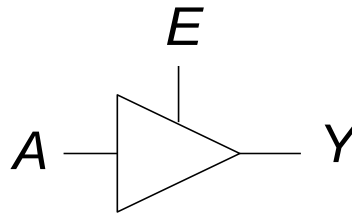

$E$	$A$	$Y$
0	0	Z
0	1	Z
1	0	0
1	1	1
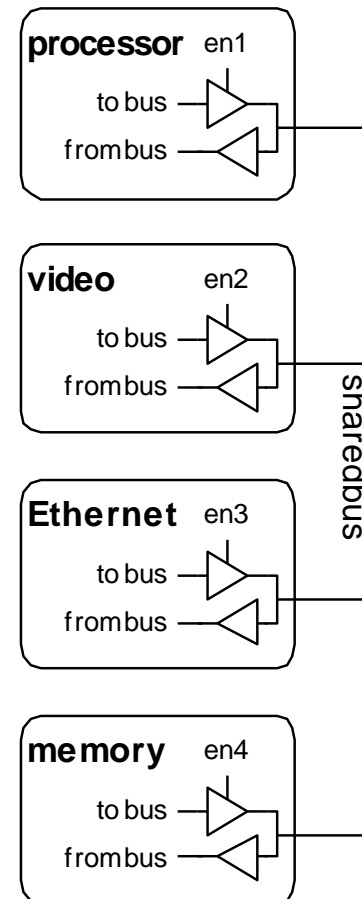
# Tristate Busses

- Floating nodes are used in tristate busses
  - Many different drivers
  - Exactly one is active at once



# Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- $PA + PA = P$
- K-maps minimize equations graphically

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Y C	AB			
	00	01	11	10
0	1	0	0	0
1	1	0	0	0

Y C	AB			
	00	01	11	10
0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

# K-Map

- Circle 1's in adjacent squares
- In Boolean expression, include only literals whose true and complement forms are *not* in the circle

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
C	Y	00	01	11	10
		0	1	0	0
		1	1	0	0

$$Y = \bar{A}\bar{B}$$