

# Lesson 7

## *Digital Logic*

---

Junying Chen

# Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- $PA + PA = P$
- K-maps minimize equations graphically

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

| Y<br>C | AB |    |    |    |
|--------|----|----|----|----|
|        | 00 | 01 | 11 | 10 |
| 0      | 1  | 0  | 0  | 0  |
| 1      | 1  | 0  | 0  | 0  |

| Y<br>C | AB                      |                   |             |                   |
|--------|-------------------------|-------------------|-------------|-------------------|
|        | 00                      | 01                | 11          | 10                |
| 0      | $\bar{A}\bar{B}\bar{C}$ | $\bar{A}B\bar{C}$ | $AB\bar{C}$ | $A\bar{B}\bar{C}$ |
| 1      | $\bar{A}\bar{B}C$       | $\bar{A}BC$       | $ABC$       | $A\bar{B}C$       |

# K-Map

- Circle 1's in adjacent squares
- In Boolean expression, include only literals whose true and complement forms are *not* in the circle

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

|   |   | AB |    |    |    |
|---|---|----|----|----|----|
| C | Y | 00 | 01 | 11 | 10 |
|   |   | 0  | 1  | 0  | 0  |
| 1 |   | 1  | 1  | 0  | 0  |

$$Y = \bar{A}\bar{B}$$

# 3-Input K-Map

| Y<br>C \ AB |                         | 00 |                   | 01 |                   | 11 |             | 10 |  |
|-------------|-------------------------|----|-------------------|----|-------------------|----|-------------|----|--|
|             |                         |    |                   |    |                   |    |             |    |  |
| 0           | $\bar{A}\bar{B}\bar{C}$ |    | $\bar{A}B\bar{C}$ |    | $A\bar{B}\bar{C}$ |    | $ABC$       |    |  |
|             | $\bar{A}\bar{B}C$       |    | $\bar{A}BC$       |    | $ABC$             |    | $A\bar{B}C$ |    |  |

Truth Table

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

**K-Map**

| $Y$<br>$C \backslash AB$ |  | 00 | 01 | 11 | 10 |
|--------------------------|--|----|----|----|----|
|                          |  | 00 | 01 | 11 | 10 |
| 0                        |  | 0  | 1  | 0  | 0  |
| 1                        |  | 0  | 1  | 1  | 0  |

# 3-Input K-Map

| Y<br>C | AB                |                   |             |                   |
|--------|-------------------|-------------------|-------------|-------------------|
|        | 00                | 01                | 11          | 10                |
| 0      | $ABC$             | $\bar{A}BC$       | $AB\bar{C}$ | $A\bar{B}\bar{C}$ |
| 1      | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $ABC$       | $A\bar{B}C$       |

Truth Table

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

*AB K-Map*

| Y<br>C | AB |    |    |    |
|--------|----|----|----|----|
|        | 00 | 01 | 11 | 10 |
| 0      | 0  | 1  | 0  | 0  |
| 1      | 0  | 1  | 1  | 0  |

*Handwritten notes:  $\bar{A}B$  (circled),  $BC$  (circled),  $\bar{A}B + BC$*


$$Y = \bar{A}B + BC$$

# K-Map Definitions

- **Complement:** variable with a bar over it  
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement  
 $\bar{A}, A, \bar{B}, B, C, \bar{C}$
- **Implicant:** product of literals  
 $A\bar{B}C, \bar{A}C, BC$
- **Prime implicant:** implicant corresponding to the largest circle in a K-map

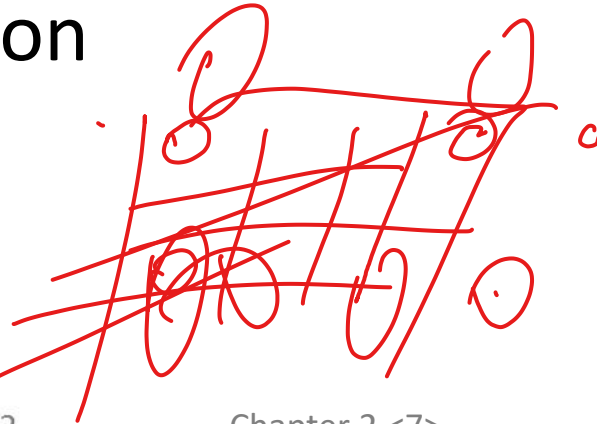
# K-Map Circling Rules

- Every 1 must be circled at least once
- Each circle must span a power of 2 (i.e. 1, 2, 4) squares in each direction
- Each circle must be as large as possible
- A circle may wrap around the edges
- A “don't care” (X) is circled only if it helps minimize the equation



# 4-Input K-Map

| A | B | C | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

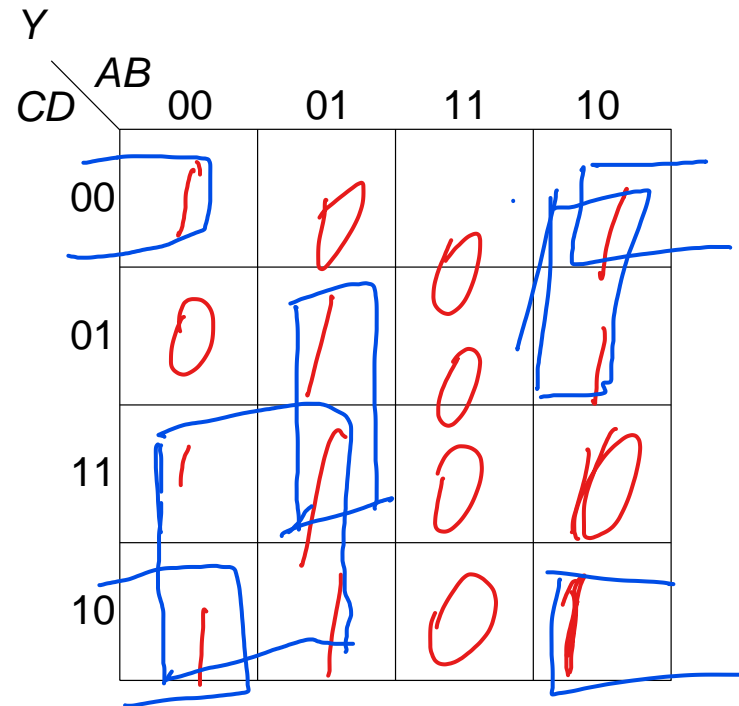



# 4-Input K-Map

| A | B | C | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

|    |    | AB |    |    |    |
|----|----|----|----|----|----|
|    |    | 00 | 01 | 11 | 10 |
| CD | 00 | 1  | 0  | 0  | 1  |
|    | 01 | 0  | 1  | 0  | 1  |
|    | 11 | 1  | 1  | 0  | 0  |
|    | 10 | 1  | 1  | 0  | 1  |

# 4-Input K-Map


| A | B | C | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

| Y<br>CD \ AB | AB |    |    |    |
|--------------|----|----|----|----|
|              | 00 | 01 | 11 | 10 |
| 00           | 1  | 0  | 0  | 1  |
| 01           | 1  | 1  | 0  | 1  |
| 11           | 1  | 1  | 0  | 0  |
| 10           | 1  | 1  | 0  | 1  |

$$Y = \bar{A}\bar{C} + \bar{A}BD + A\bar{B}\bar{C} + \bar{B}\bar{D}$$

# K-Maps with Don't Cares

| A | B | C | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | X |
| 1 | 0 | 1 | 1 | X |
| 1 | 1 | 0 | 0 | X |
| 1 | 1 | 0 | 1 | X |
| 1 | 1 | 1 | 0 | X |
| 1 | 1 | 1 | 1 | X |

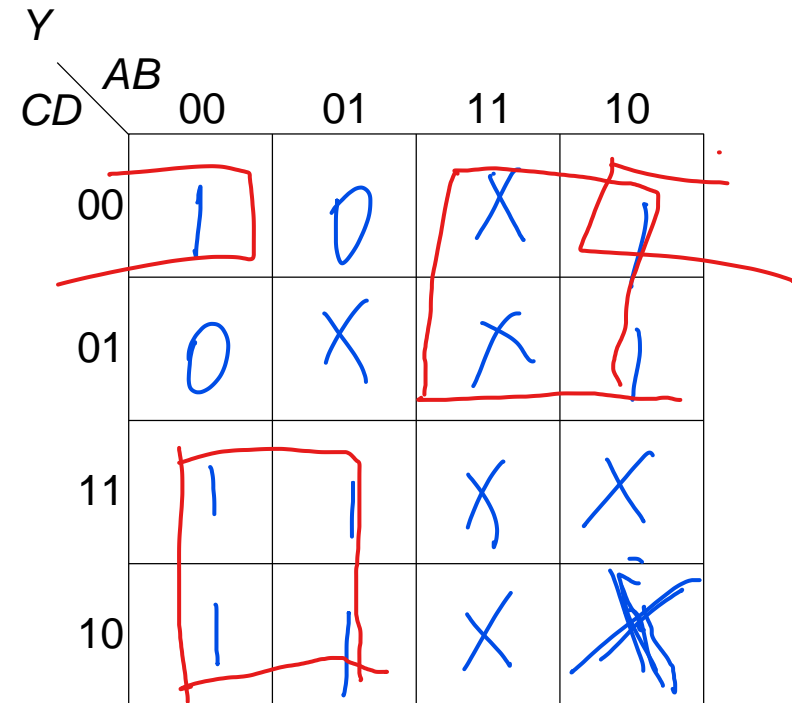

# K-Maps with Don't Cares

| A | B | C | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | X |
| 1 | 0 | 1 | 1 | X |
| 1 | 1 | 0 | 0 | X |
| 1 | 1 | 0 | 1 | X |
| 1 | 1 | 1 | 0 | X |
| 1 | 1 | 1 | 1 | X |

|   |    | AB |    |    |    |
|---|----|----|----|----|----|
| Y | CD | 00 | 01 | 11 | 10 |
|   |    | 00 | 01 | 11 | 10 |
|   | 00 | 1  | 0  | X  | 1  |
|   | 01 | 0  | X  | X  | 1  |
|   | 11 | 1  | 1  | X  | X  |
|   | 10 | 1  | 1  | X  | X  |

# K-Maps with Don't Cares

| A | B | C | D | Y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | X |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | X |
| 1 | 0 | 1 | 1 | X |
| 1 | 1 | 0 | 0 | X |
| 1 | 1 | 0 | 1 | X |
| 1 | 1 | 1 | 0 | X |
| 1 | 1 | 1 | 1 | X |

$AB\bar{C}D$   
 $AB\bar{C}\bar{D}$

| Y<br>CD \ AB | 00 | 01 | 11 | 10 |
|--------------|----|----|----|----|
| 00           | 1  | 0  | X  | 1  |
| 01           | 0  | X  | X  | 1  |
| 11           | 1  | 1  | X  | X  |
| 10           | 1  | 1  | X  | X  |

$$Y = A + \bar{B}\bar{D} + C$$


# Combinational Building Blocks

- Multiplexers
- Decoders

# Multiplexer (Mux)

- Selects between one of  $N$  inputs to connect to output
- $\log_2 N$ -bit select input – control input
- Example:

## 2:1 Mux

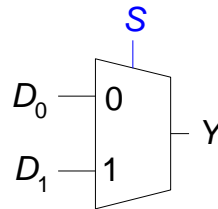

| $S$ | $D_1$ | $D_0$ | $Y$ |
|-----|-------|-------|-----|
| 0   | 0     | 0     | 0   |
| 0   | 0     | 1     | 1   |
| 0   | 1     | 0     | 0   |
| 0   | 1     | 1     | 1   |
| 1   | 0     | 0     | 0   |
| 1   | 0     | 1     | 0   |
| 1   | 1     | 0     | 1   |
| 1   | 1     | 1     | 1   |

| $S$ | $Y$   |
|-----|-------|
| 0   | $D_0$ |
| 1   | $D_1$ |


# Multiplexer Implementations

## Logic gates

- Sum-of-products form


| Y<br>S | $D_0 D_1$ |    |    |    |
|--------|-----------|----|----|----|
|        | 00        | 01 | 11 | 10 |
| 0      | 0         | 0  | 1  | 1  |
| 1      | 0         | 1  | 1  | 0  |

$$Y = D_0 \bar{S} + D_1 S$$

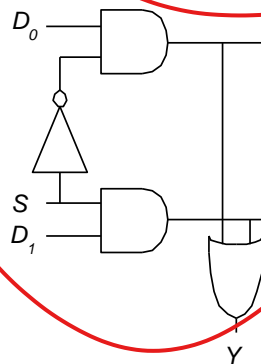
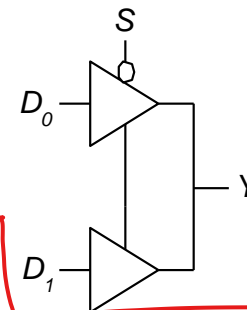
## Tristates

- For an N-input mux, use N tristates
- Turn on exactly one to select the appropriate input






# Logic using Multiplexers

- Using the mux as a **lookup table**


| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

$$Y = AB$$

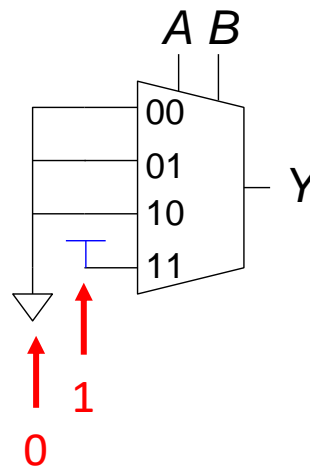


# Logic using Multiplexers

- Reducing the size of the mux

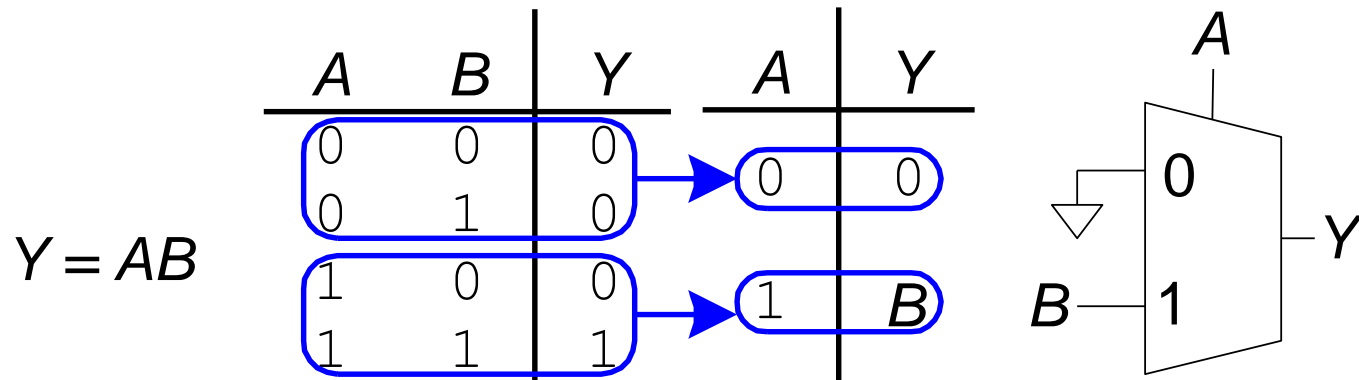

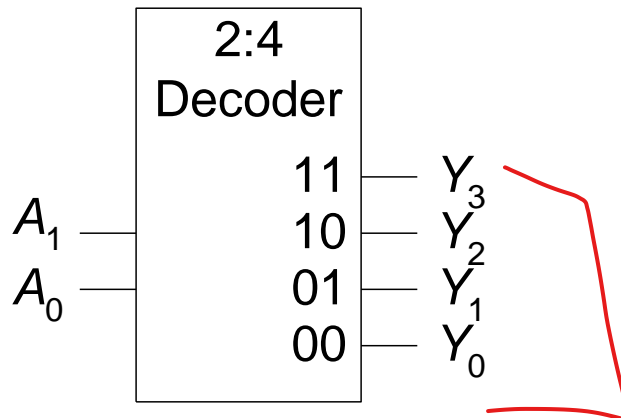
# Decoders

- $N$  inputs,  $2^N$  outputs
- One-hot outputs: only one output HIGH at once




| $A_1$ | $A_0$ | $Y_3$ | $Y_2$ | $Y_1$ | $Y_0$ |
|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     | 1     |
| 0     | 1     | 0     | 0     | 1     | 0     |
| 1     | 0     | 0     | 1     | 0     | 0     |
| 1     | 1     | 1     | 0     | 0     | 0     |

# Decoder Implementation

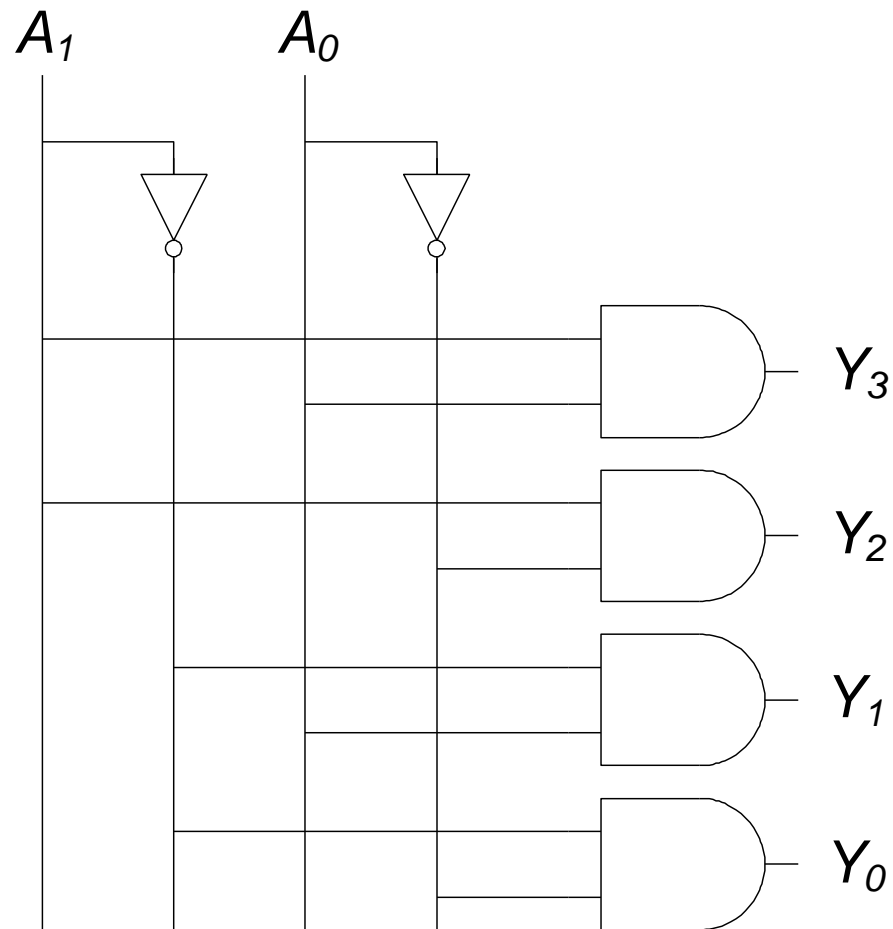


# Logic Using Decoders

- OR minterms

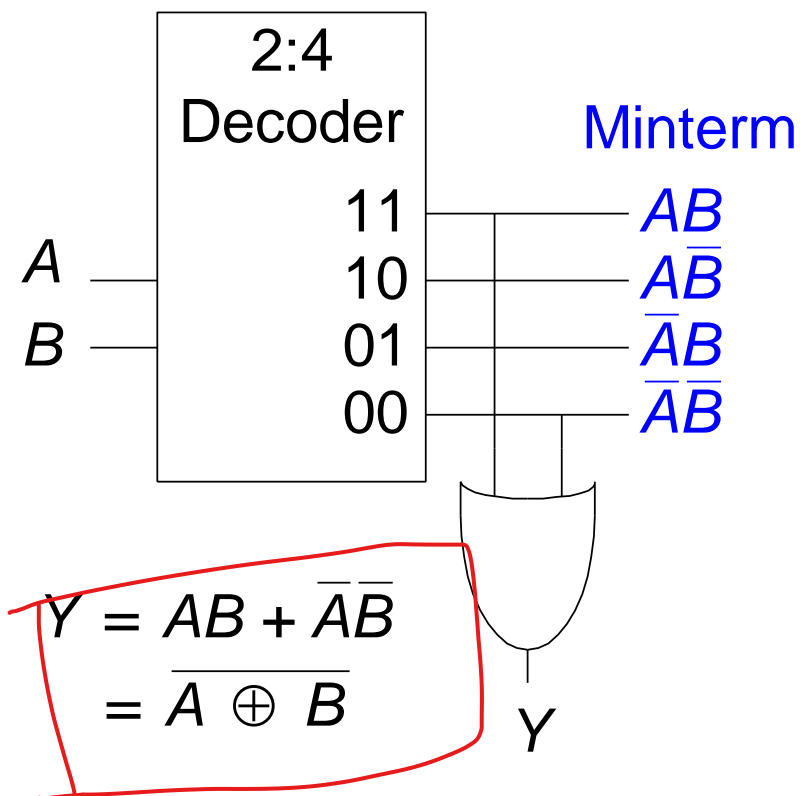

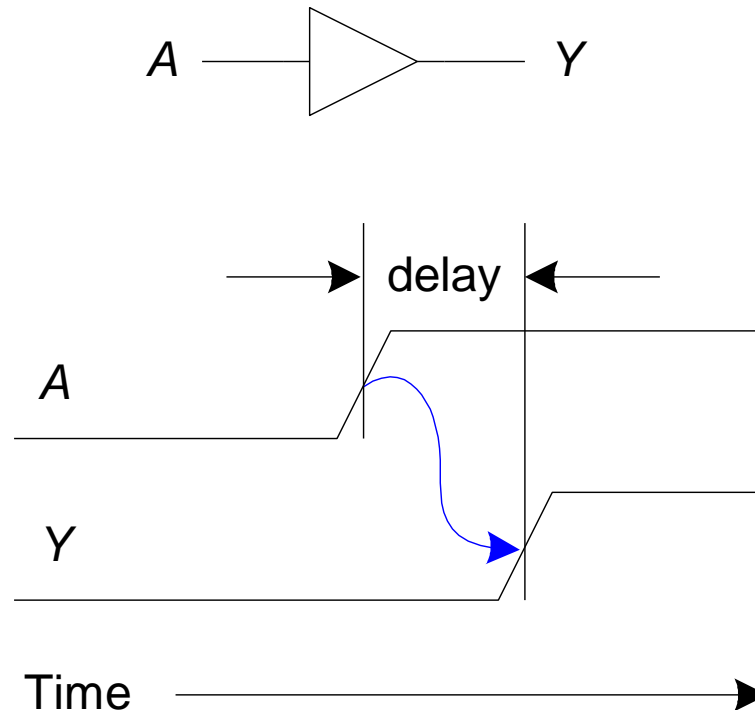
# Timing

- Delay between input change and output change
- How to build fast circuits?


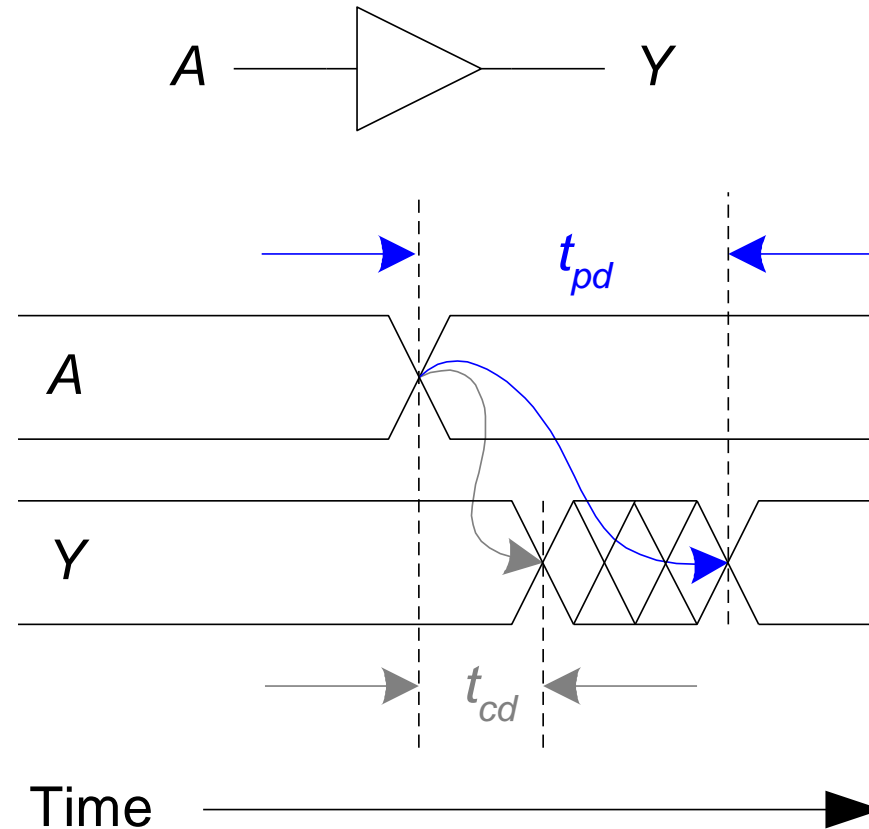
# Propagation & Contamination Delay

- **Propagation delay:**  $t_{pd}$  = max delay from input to output
- **Contamination delay:**  $t_{cd}$  = min delay from input to output




# Propagation & Contamination Delay

- Delay is caused by
  - Capacitance and resistance in a circuit
  - Speed of light limitation
- Reasons why  $t_{pd}$  and  $t_{cd}$  may be different:
  - Different rising and falling delays
  - Multiple inputs and outputs, some of which are faster than others
  - Circuits slow down when hot and speed up when cold





# Critical (Long) & Short Paths

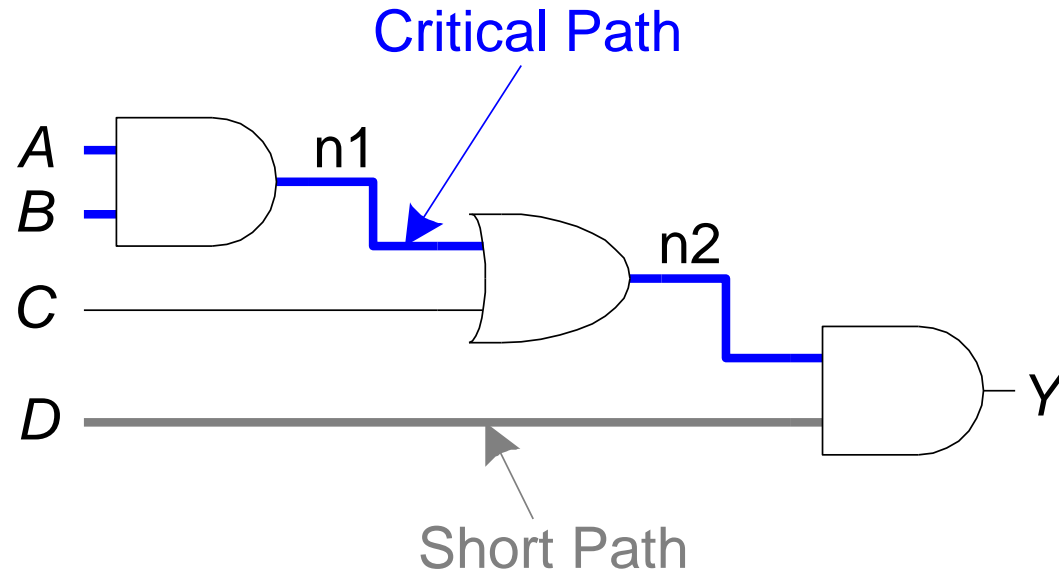

**Critical (Long) Path:**  $t_{pd} = 2t_{pd\_AND} + t_{pd\_OR}$

**Short Path:**  $t_{cd} = t_{cd\_AND}$


After-class reading: Example 2.15 and 2.16 in Textbook

# Glitches

- When a single input change causes an output to change multiple times
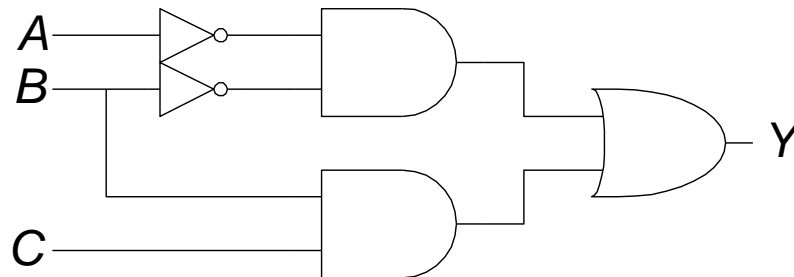
# Glitch Example



- What happens when  $A = 0$ ,  $C = 1$ ,  $B$  falls?





|     |   | $AB$ |    |    |    |
|-----|---|------|----|----|----|
|     |   | 00   | 01 | 11 | 10 |
| $C$ | 0 | 1    | 0  | 0  | 0  |
|     | 1 | 1    | 1  | 1  | 0  |

$$Y = \bar{A}\bar{B} + BC$$

# Glitch Example (cont.)

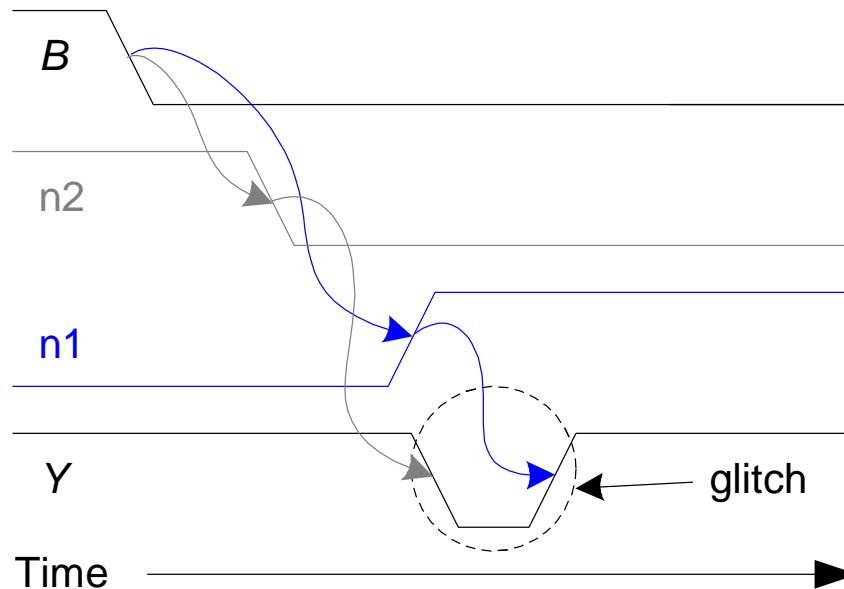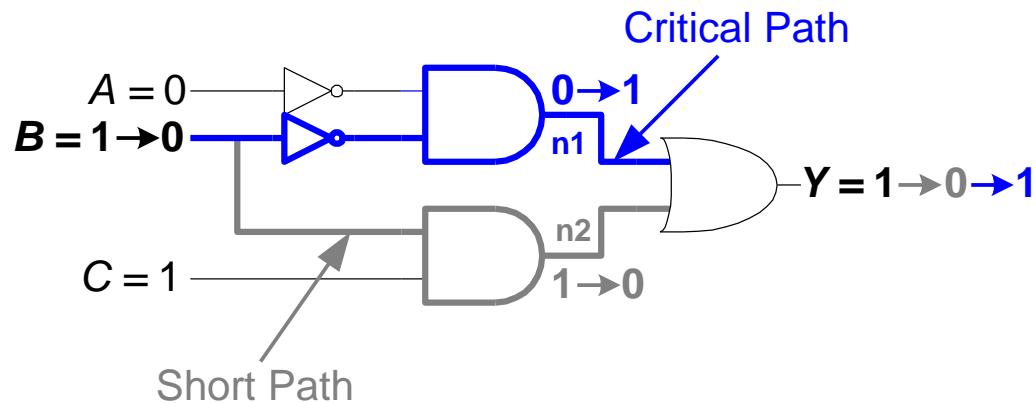

# Fixing the Glitch

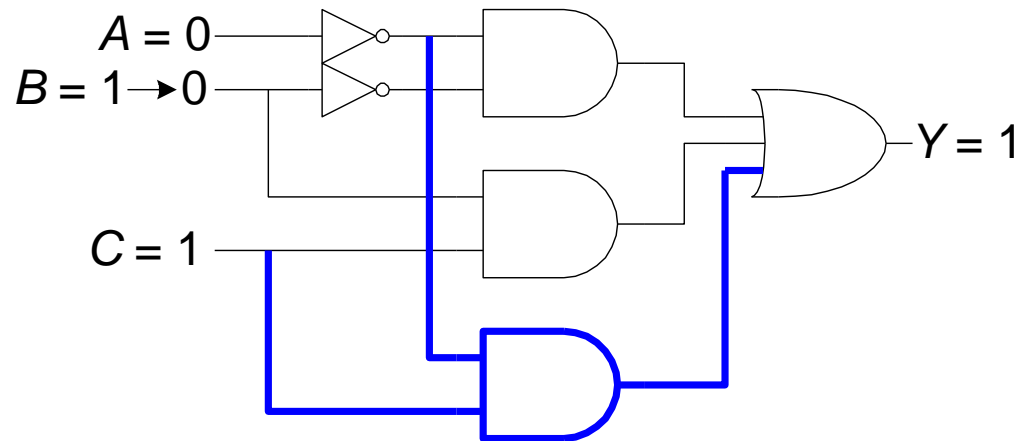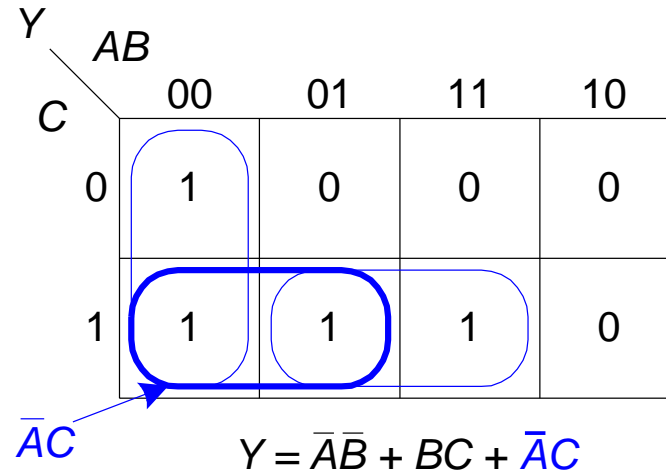

# Why Understand Glitches?

- Glitches don't cause problems because of **synchronous design** conventions (see Chapter 3)
- It's important to **recognize** a glitch: in simulations or on oscilloscope
- Can't get rid of all glitches – simultaneous transitions on multiple inputs can also cause glitches