 


# CHAPTER 3


**Exercise 3.1**

---




**Exercise 3.3**

---

 

### Exercise 3.5

---

 


### Exercise 3.7

---

The circuit is sequential because it involves feedback and the output depends on previous values of the inputs. This is a SR latch. When  $\bar{S} = 0$  and  $\bar{R} = 1$ , the circuit sets  $Q$  to 1. When  $\bar{S} = 1$  and  $\bar{R} = 0$ , the circuit resets  $Q$  to 0. When both  $\bar{S}$  and  $\bar{R}$  are 1, the circuit remembers the old value. And when both  $\bar{S}$  and  $\bar{R}$  are 0, the circuit drives both outputs to 1.

### Exercise 3.9

---

 


### Exercise 3.11


---

If  $A$  and  $B$  have the same value,  $C$  takes on that value. Otherwise,  $C$  retains its old value.

### Exercise 3.13

 

### Exercise 3.15

 

### Exercise 3.17

If N is even, the circuit is stable and will not oscillate.

### Exercise 3.19

The system has at least five bits of state to represent the 24 floors that the elevator might be on.

### Exercise 3.21

The FSM could be factored into four independent state machines, one for each student. Each of these machines has five states and requires 3 bits, so at least 12 bits of state are required for the factored design.

**Exercise 3.23**

---

This finite state machine asserts the output  $Q$  when  $A$  AND  $B$  is TRUE.

state	encoding $s_{1:0}$
S0	00
S1	01
S2	10

TABLE 3.1 State encoding for Exercise 3.23


current state		inputs		next state		output
$s_1$	$s_0$	$a$	$b$	$s'_1$	$s'_0$	$q$
0	0	0	X	0	0	0
0	0	1	X	0	1	0
0	1	X	0	0	0	0
0	1	X	1	1	0	0
1	0	1	1	1	0	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0

TABLE 3.2 Combined state transition and output table with binary encodings for Exercise 3.23


$$S'_1 = \overline{S_1}S_0B + S_1AB$$

$$S'_0 = \overline{S_1}\overline{S_0}A$$

$$Q' = S_1AB$$

 

Exercise 3.25

 

state	encoding $s_1:0$
S0	000
S1	001

TABLE 3.3 State encoding for Exercise 3.25

state	encoding $s_{1:0}$
S2	010
S3	100
S4	101

TABLE 3.3 State encoding for Exercise 3.25

current state			input	next state			output
$s_2$	$s_1$	$s_0$	$a$	$s'_2$	$s'_1$	$s'_0$	$q$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	0
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	1
1	0	1	0	1	0	0	1
1	0	1	1	1	0	1	0


TABLE 3.4 Combined state transition and output table with binary encodings for Exercise 3.25

$$S'_2 = \overline{S_2}S_1\overline{S_0} + S_2\overline{S_1}S_0$$

$$S'_1 = \overline{S_2}\overline{S_1}S_0A$$

$$S'_0 = A(\overline{S_2}\overline{S_0} + S_2\overline{S_1})$$
 
$$Q = S_2\overline{S_1}\overline{S_0}A + S_2\overline{S_1}S_0\overline{A}$$



### Exercise 3.27

---

 


FIGURE 3.1 State transition diagram for Exercise 3.27



current state $s_{2:0}$	next state $s'_{2:0}$
000	001
001	011
011	010
010	110
110	111
111	101
101	100
100	000

TABLE 3.5 State transition table for Exercise 3.27

$$\begin{aligned} S'_2 &= S_1 \overline{S_0} + S_2 S_0 \\ S'_1 &= \overline{S_2} S_0 + S_1 \overline{S_0} \\ S'_0 &= \overline{S_2 \oplus S_1} \\ Q_2 &= S_2 \\ Q_1 &= S_1 \\ Q_0 &= S_0 \end{aligned}$$

 


FIGURE 3.2 Hardware for Gray code counter FSM for Exercise 3.27

**Exercise 3.29**

 


FIGURE 3.3 Waveform showing Z output for Exercise 3.29

(b) This FSM is a Mealy FSM because the output depends on the current value of the input as well as the current state.

(c)

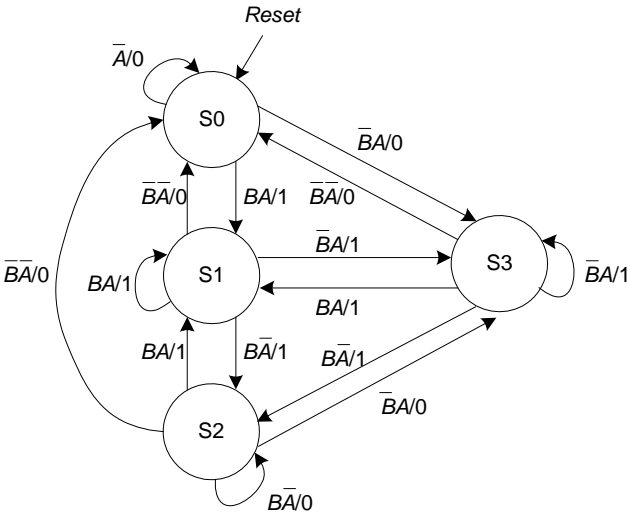


FIGURE 3.4 State transition diagram for Exercise 3.29

(Note: another viable solution would be to allow the state to transition from S0 to S1 on  $\overline{B}\overline{A}/0$ . The arrow from S0 to S0 would then be  $\overline{B}\overline{A}/0$ .)

current state $s_{1:0}$	inputs		next state $s'_{1:0}$	output $z$
	$b$	$a$		
00	X	0	00	0
00	0	1	11	0
00	1	1	01	1
01	0	0	00	0
01	0	1	11	1
01	1	0	10	1
01	1	1	01	1
10	0	X	00	0
10	1	0	10	0

TABLE 3.6 State transition table for Exercise 3.29

current state $s_{1:0}$	inputs		next state $s'_{1:0}$	output $z$
	$b$	$a$		
10	1	1	01	1
11	0	0	00	0
11	0	1	11	1
11	1	0	10	1
11	1	1	01	1

TABLE 3.6 State transition table for Exercise 3.29

$$S'_1 = \overline{B}A(\overline{S_1} + S_0) + B\overline{A}(S_1 + \overline{S_0})$$

$$S'_0 = A(\overline{S_1} + S_0 + B)$$

$$Z = BA + S_0(A + B)$$

 


FIGURE 3.5 Hardware for FSM of Exercise 3.26

**Note:** One could also build this functionality by registering input A, producing both the logical AND and OR of input A and its previous (registered)

value, and then muxing the two operations using  $B$ . The output of the mux is  $Z$ :  
 $Z = A\text{Aprev}$  (if  $B = 0$ );  $Z = A + A\text{prev}$  (if  $B = 1$ ).

**Exercise 3.31**

---


This finite state machine is a divide-by-two counter (see Section 3.4.2) when  $X = 0$ . When  $X = 1$ , the output,  $Q$ , is HIGH.

current state		input	next state	
$s_1$	$s_0$	$x$	$s'_1$	$s'_0$
0	0	0	0	1
0	0	1	1	1
0	1	0	0	0
0	1	1	1	0
1	X	X	0	1

TABLE 3.7 State transition table with binary encodings for Exercise 3.31

current state		output
$s_1$	$s_0$	$q$
0	0	0
0	1	1
1	X	1

TABLE 3.8 Output table for Exercise 3.31

 

### Exercise 3.33

(a) First, we calculate the propagation delay through the combinational logic:

$$\begin{aligned}
 t_{pd} &= 3t_{pd\_XOR} \\
 &= 3 \times 100 \text{ ps} \\
 &= \mathbf{300 \text{ ps}}
 \end{aligned}$$

Next, we calculate the cycle time:

$$\begin{aligned}
 T_c &\geq t_{pcq} + t_{pd} + t_{\text{setup}} \\
 &\geq [70 + 300 + 60] \text{ ps} \\
 &= 430 \text{ ps} \\
 f &= 1 / 430 \text{ ps} = \mathbf{2.33 \text{ GHz}}
 \end{aligned}$$

(b)

$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}} + t_{\text{skew}}$$

Thus,

$$\begin{aligned}
 t_{\text{skew}} &\leq T_c - (t_{pcq} + t_{pd} + t_{\text{setup}}), \text{ where } T_c = 1 / 2 \text{ GHz} = 500 \text{ ps} \\
 &\leq [500 - 430] \text{ ps} = \mathbf{70 \text{ ps}}
 \end{aligned}$$

(c)

First, we calculate the contamination delay through the combinational logic:

$$\begin{aligned}
 t_{cd} &= t_{cd\_XOR} \\
 &= 55 \text{ ps}
 \end{aligned}$$

$$t_{ccq} + t_{cd} > t_{\text{hold}} + t_{\text{skew}}$$

Thus,

$$\begin{aligned}
 t_{\text{skew}} &< (t_{ccq} + t_{cd}) - t_{\text{hold}} \\
 &< (50 + 55) - 20 \\
 &< \mathbf{85 \text{ ps}}
 \end{aligned}$$



$$\begin{aligned} t_{\text{skew}} &< (t_{ccq} + t_{cd\_CLB}) - t_{\text{hold}} \\ &< [(0.5 + 0.3) - 0] \text{ ns} \\ &< \mathbf{0.8 \text{ ns} = 800 \text{ ps}} \end{aligned}$$

### Exercise 3.37

---

$$P(\text{failure})/\text{sec} = 1/\text{MTBF} = 1/(50 \text{ years} * 3.15 \times 10^7 \text{ sec/year}) = \mathbf{6.34 \times 10^{-10}} \quad (\text{EQ 3.26})$$

$$P(\text{failure})/\text{sec} \text{ waiting for one clock cycle: } N * (T_0/T_c) * e^{-(T_c - t_{\text{setup}})/\text{Tau}}$$

$$= 0.5 * (110/1000) * e^{-(1000-70)/100} = 5.0 \times 10^{-6}$$

$$P(\text{failure})/\text{sec} \text{ waiting for two clock cycles: } N * (T_0/T_c) * [e^{-(T_c - t_{\text{setup}})/\text{Tau}}]^2$$

$$= 0.5 * (110/1000) * [e^{-(1000-70)/100}]^2 = 4.6 \times 10^{-10}$$

This is just less than the required probability of failure ( $6.34 \times 10^{-10}$ ). Thus, **2 cycles** of waiting is just adequate to meet the MTBF.

### Exercise 3.39

---

We assume a two flip-flop synchronizer. The most significant impact on the probability of failure comes from the exponential component. If we ignore the  $T_0/T_c$  term in the probability of failure equation, assuming it changes little with increases in cycle time, we get:

$$\begin{aligned} P(\text{failure}) &= e^{-\frac{t}{\tau}} \\ \text{MTBF} &= \frac{1}{P(\text{failure})} = e^{\frac{T_c - t_{\text{setup}}}{\tau}} \\ \frac{\text{MTBF}_2}{\text{MTBF}_1} &= 10 = e^{\frac{T_{c2} - T_{c1}}{30 \text{ ps}}} \end{aligned}$$

Solving for  $T_{c2} - T_{c1}$ , we get:

$$T_{c2} - T_{c1} = 69 \text{ ps}$$



Thus, the clock cycle time must increase by **69 ps**. This holds true for cycle times much larger than  $T_0$  (20 ps) and the increased time (69 ps).

### Question 3.1

 


FIGURE 3.7 State transition diagram for Question 3.1

current state $s_{5:0}$	input	next state $s'_{5:0}$
	$a$	
000001	0	000010
000001	1	000001
000010	0	000010
000010	1	000100
000100	0	001000
000100	1	000001
001000	0	000010
001000	1	010000
010000	0	100000
010000	1	000001
100000	0	000010
100000	1	000001

TABLE 3.9 State transition table for Question 3.1

$S'_5 = S_4A$   
 $S'_4 = S_3A$   
 $S'_3 = S_2A$   
 $S'_2 = S_1A$   
 $S'_1 = A(S_1 + S_3 + S_5)$   
 $S'_0 = A(S_0 + S_2 + S_4 + S_5)$   
 $Q = S_5$

 



FIGURE 3.8 Finite state machine hardware for Question 3.1

### Question 3.3

A latch allows input  $D$  to flow through to the output  $Q$  when the clock is HIGH. A flip-flop allows input  $D$  to flow through to the output  $Q$  at the clock edge. A flip-flop is preferable in systems with a single clock. Latches are preferable in *two-phase clocking* systems, with two clocks. The two clocks are used to eliminate system failure due to hold time violations. Both the phase and frequency of each clock can be modified independently.

**Question 3.5**

---

 

**FIGURE 3.9** State transition diagram for edge detector circuit of Question 3.5

current state $s_{1:0}$	input	next state $s'_{1:0}$
	$a$	
00	0	00
00	1	01
01	0	00
01	1	10
10	0	00
10	1	10

**TABLE 3.10** State transition table for Question 3.5

$$S'_1 = AS_1$$
$$S'_0 = AS_1S_0$$

$$Q = S_1$$

 


FIGURE 3.10 Finite state machine hardware for Question 3.5

### Question 3.7

A flip-flop with a negative hold time allows  $D$  to start changing *before* the clock edge arrives.

### Question 3.9

Without the added buffer, the propagation delay through the logic,  $t_{pd}$ , must be less than or equal to  $T_c - (t_{pcq} + t_{setup})$ . However, if you add a buffer to the clock input of the receiver, the clock arrives at the receiver later. The earliest that the clock edge arrives at the receiver is  $t_{cd\_BUF}$  after the actual clock edge. Thus, the propagation delay through the logic is now given an extra  $t_{cd\_BUF}$ . So,  $t_{pd}$  now must be less than  $T_c + t_{cd\_BUF} - (t_{pcq} + t_{setup})$ .

