

Computer Organization & Architecture

## 2-3 Ripple-Carry Adder & Addition/Subtraction Logic Unit

Guohua Wang

School of Software Engineering

# Contents of this lecture

- 1-bit Full Adder
- n-bit Ripple-Carry Adder
- Hierarchical Adder
- Addition/Subtraction Logic Unit

# 1-bit Full Adder (1)

- Full Adder

- A **full adder** circuit takes three bits of input, and produces a two-bit output consisting of a sum and a carry out.

 


Figure 9.2 (a) Logic for a single stage

# 1-bit Full Adder (2)

- Logic Truth Table


| $x_i$ | $y_i$ | $c_i$ | $s_i$ | $c_{i+1}$ |
|-------|-------|-------|-------|-----------|
| 0     | 0     | 0     | 0     | 0         |
| 0     | 0     | 1     | 1     | 0         |
| 0     | 1     | 0     | 1     | 0         |
| 0     | 1     | 1     | 0     | 1         |
| 1     | 0     | 0     | 1     | 0         |
| 1     | 0     | 1     | 0     | 1         |
| 1     | 1     | 0     | 0     | 1         |
| 1     | 1     | 1     | 1     | 1         |

# 1-bit Full Adder (3)

- Logic Expressions and Logic Figures

–  $S_i$
 
$$\begin{aligned} S_i &= \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i \\ &= x_i \oplus y_i \oplus c_i \end{aligned}$$




# 1-bit Full Adder (4)

- Logic Expressions and Logic Figures (ctd.)

–  $c_{i+1}$

 
$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$


 
# n-bit Ripple-Carry Adder (1)


- A 4-bit Adder

- Four full adders together make a 4-bit adder.
- There are nine total inputs:
  - Two 4-bit numbers, A3 A2 A1 A0 and B3 B2 B1 B0
  - An initial carry in, CI
- The five outputs are:
  - A 4-bit sum, S3 S2 S1 S0
  - A carry out, CO



# n-bit Ripple-Carry Adder (2)


- A 4-bit Adder

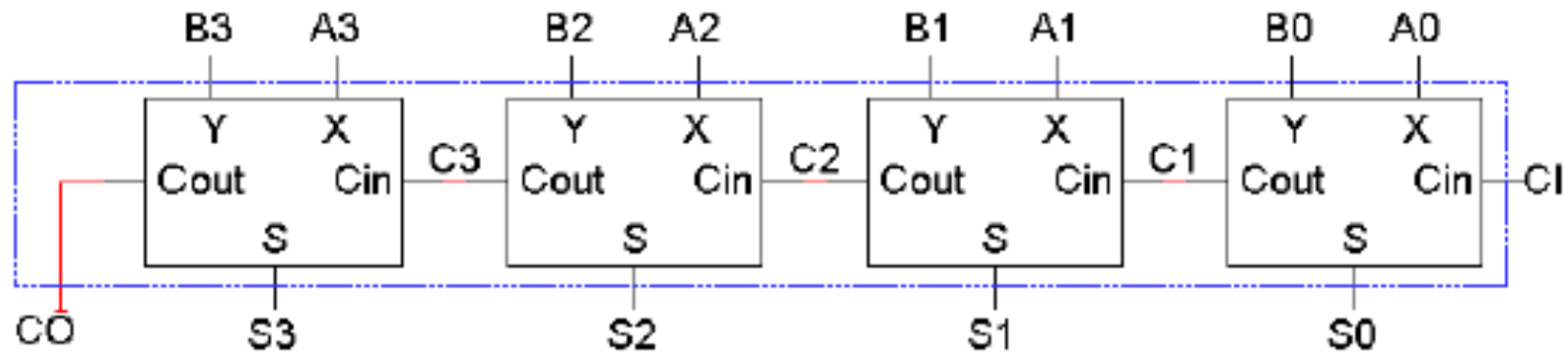


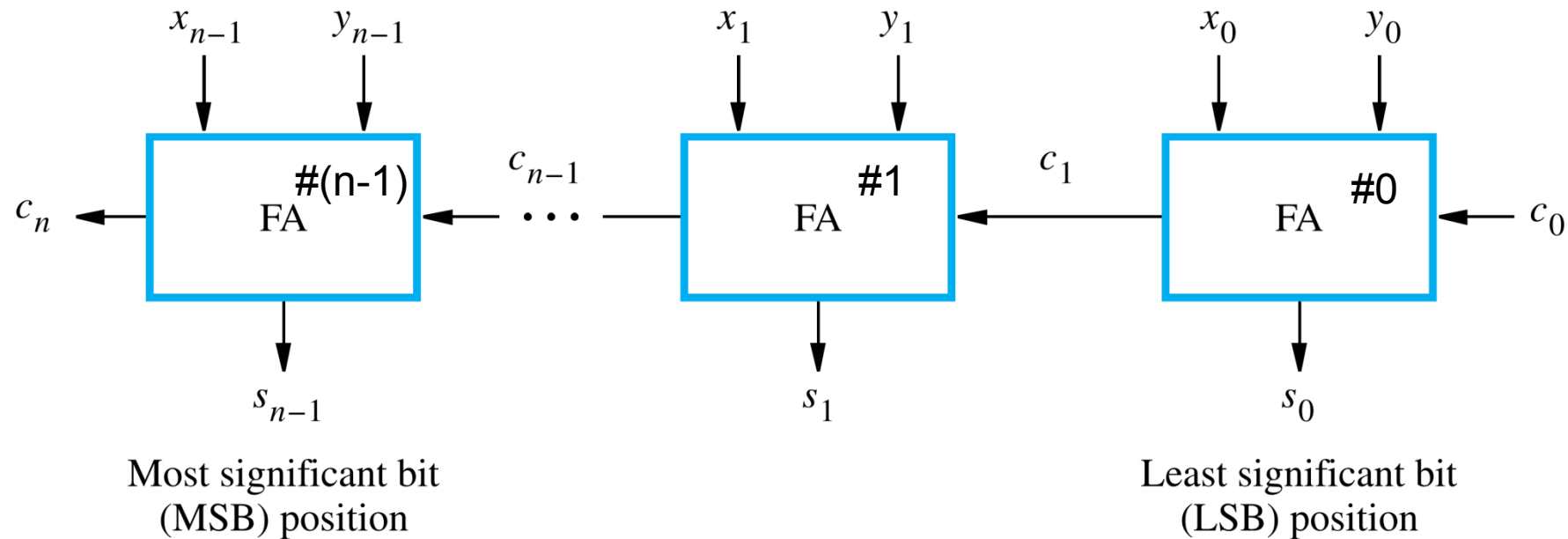
# n-bit Ripple-Carry Adder (3)

- Organization of  $n$ -bit Ripple-Carry Adder



Input:  $X = x_{n-1} \dots x_1 x_0$   
 $Y = y_{n-1} \dots y_1 y_0$   
 $c_0$   
Output:  $S = s_{n-1} \dots s_1 s_0$   
 $c_n$

Figure 9.2 (b) An  $n$ -bit ripple-carry adder

# n-bit Ripple-Carry Adder (4)

- Overflow Detect


- Overflow =  $x_{n-1}y_{n-1}\bar{s}_{n-1} + \bar{x}_{n-1}\bar{y}_{n-1}s_{n-1}$

- Or Overflow =  $c_n \oplus c_{n-1}$

| $x_{n-1}$ | $y_{n-1}$ | $s_{n-1}$ | Overflow |
|-----------|-----------|-----------|----------|
| 0         | 0         | 0         | 0        |
| 0         | 0         | 1         | 1        |
| 0         | 1         | 0         | 0        |
| 0         | 1         | 1         | 0        |
| 1         | 0         | 0         | 0        |
| 1         | 0         | 1         | 0        |
| 1         | 1         | 0         | 1        |
| 1         | 1         | 1         | 0        |
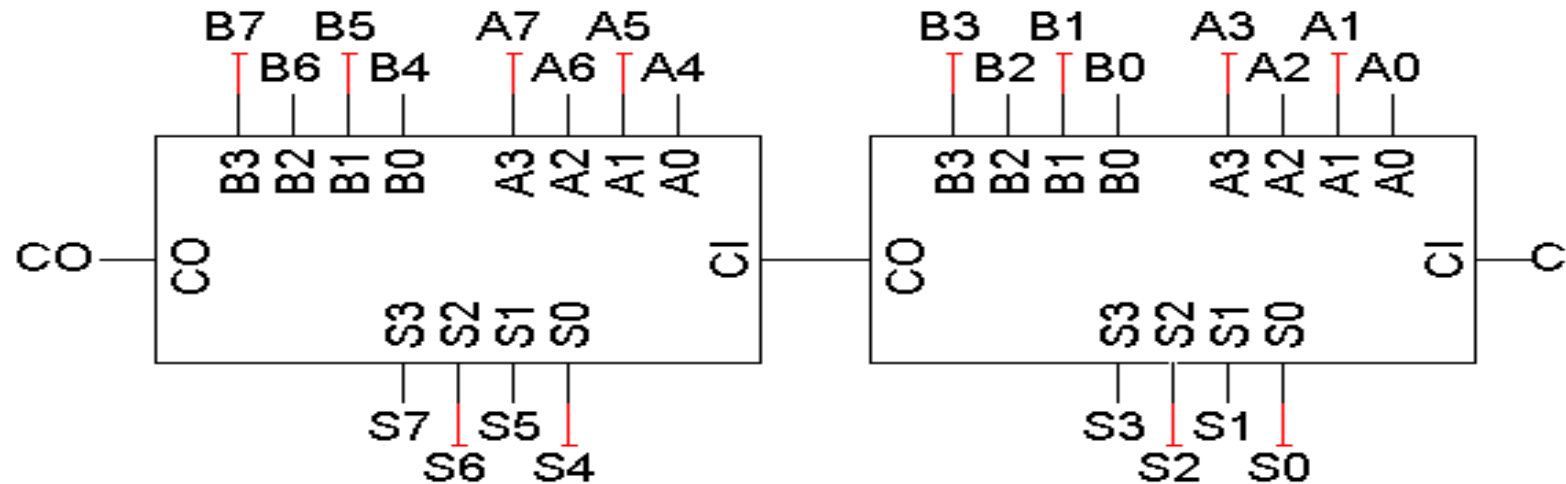
# Hierarchical Adder (1)

- Using 4-bit adders to design an 8-bit adder
  - Example Figure



A3A2A1A0: input pins of summand  
B3B2B1B0: input pins of summand  
CI: input pin of carry-in  
S3S2S1S0: output pin of sum  
CO: output pin of carry-out

# Hierarchical Adder (2)

- Using  $n$ -bit adders to design a  $kn$ -bit adder
  - Example Figure

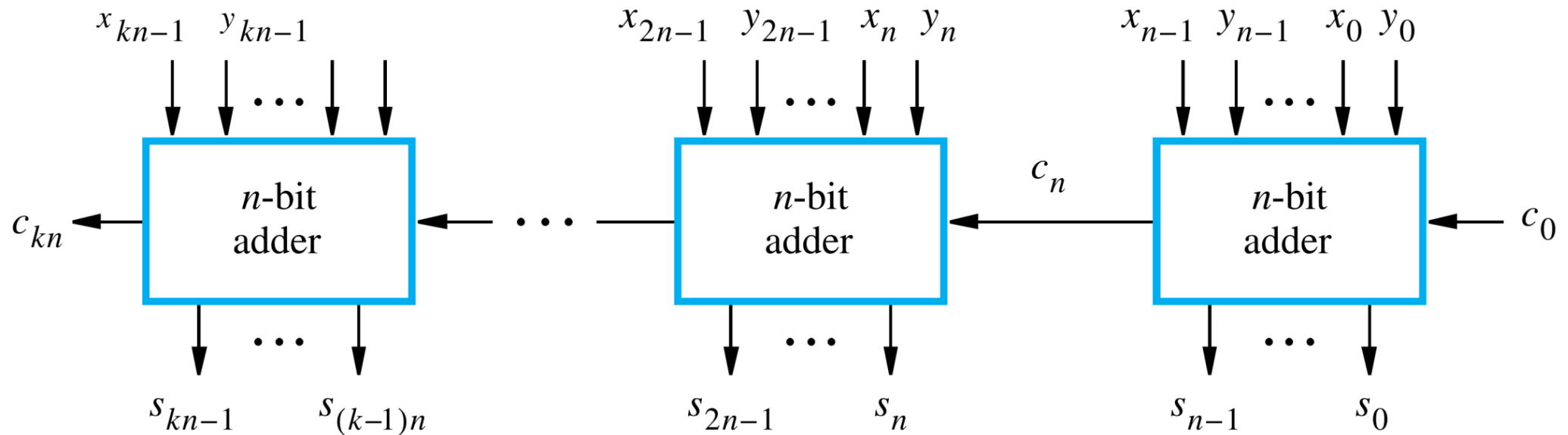




Figure 9.2 (c) Cascade of  $k$   $n$ -bit adders

# Gate Delays (1)

- Every gate takes some small fraction of a second between the time inputs are presented and the time the correct answer appears on the outputs. This little fraction of a second is called a **gate delay**.
- There are actually detailed ways of calculating gate delays that can get quite complicated, but for this class, let's just assume that there's some small constant delay that's the **same for all gates**.
  
## Gate Delays (2)

- We can use a timing diagram to show gate delays graphically.





# Propagation Delays in the Ripple Carry Adder (1)

- The delay through a network of logic gates depends on the *integrated circuit electronic technology* used in fabricating the network and on *the number of gates* in the paths from inputs to outputs.
- The delay through any combinational logic network constructed from gates in a particular technology is determined by *adding up the number of logic-gate delays along the longest signal propagation path* through the network.
- In the case of the  $n$ -bit ripple-carry adder, the longest path is from inputs  $x_0, y_0$  and  $c_0$  at the LSB position to outputs  $c_n$  and  $s_{n-1}$  at the MSB position.
 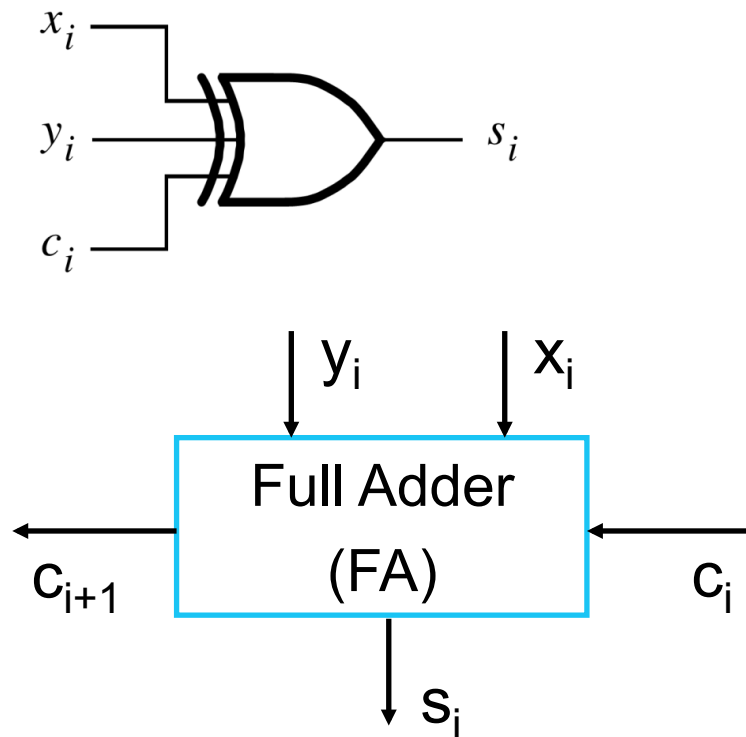
# Propagation Delays in the Ripple Carry Adder (2)


- Assume that the gate delay of an AND gate or an OR gate or a XOR gate is  $T$ .



|           |      |
|-----------|------|
| $s_i$     | $T$  |
| $c_{i+1}$ | $2T$ |


 
# Propagation Delays in the Ripple Carry Adder (3)




$$c_{n-1} \quad 2(n-1)T$$

$$s_{n-1} \quad 2(n-1)T + T = (2n-1)T$$

$$c_n \quad 2(n-1)T + 2T = (2n)T$$
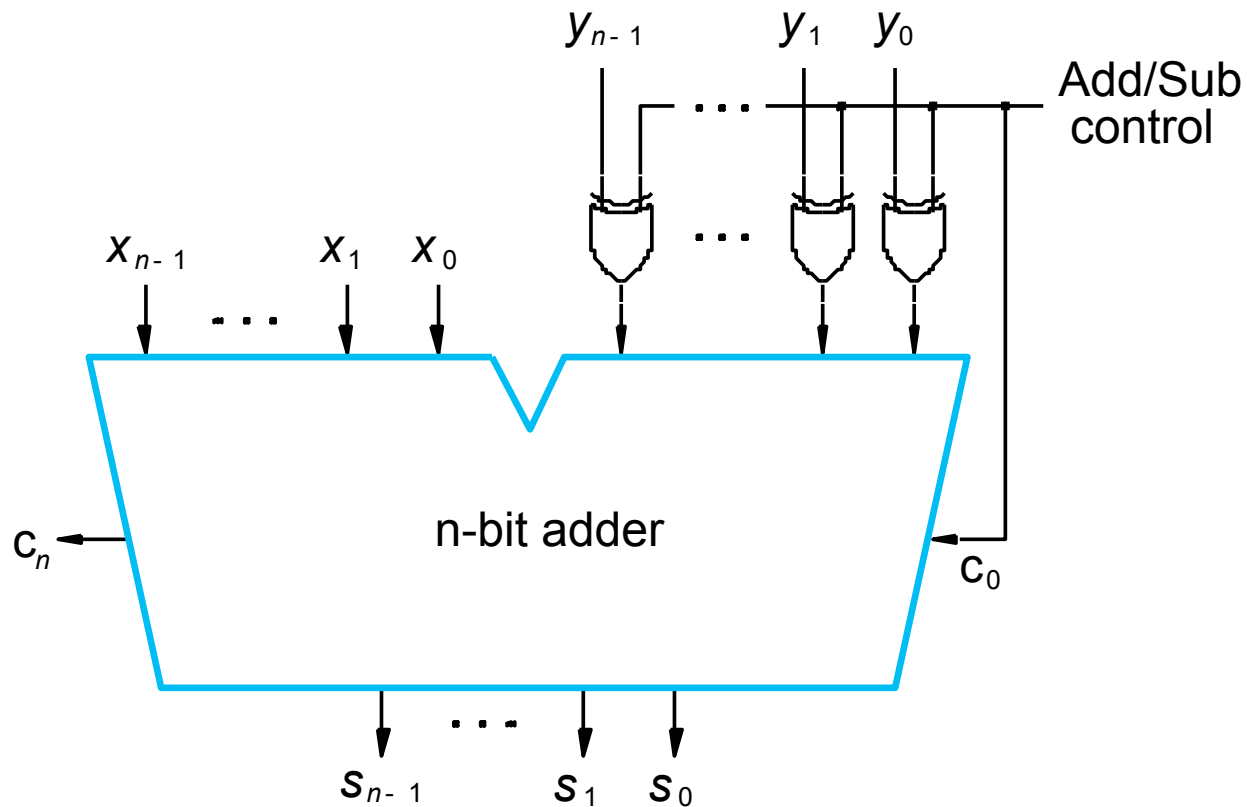
# Addition/Subtraction Logic Unit (1)

- Organization of the Addition/Subtraction Logic Unit



$$0 \oplus Y = Y$$

$$1 \oplus Y = \overline{Y}$$

Add/Sub Control=0  $c_0=0$

Perform Addition

Add/Sub Control=1  $c_0=1$

Perform Subtraction

Figure 9.3. Binary addition-subtraction logic network

## Addition/Subtraction Logic Unit (2)

- An XOR gate can be added to detect the overflow.
- All sum bits are available in  $2n$  gate delays, including the delay through the XOR gate on the Y input.

