

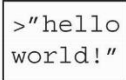


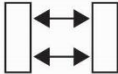
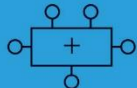
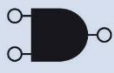
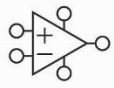
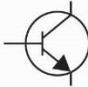

Lesson 3

Digital Logic

Junying Chen

Chapter 2 :: Topics


- Introduction
- Boolean Equations
- Boolean Algebra
- From Logic to Gates
- Multilevel Combinational Logic
- X's and Z's
- Karnaugh Maps
- Combinational Building Blocks
- Timing

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction


A logic circuit is composed of:

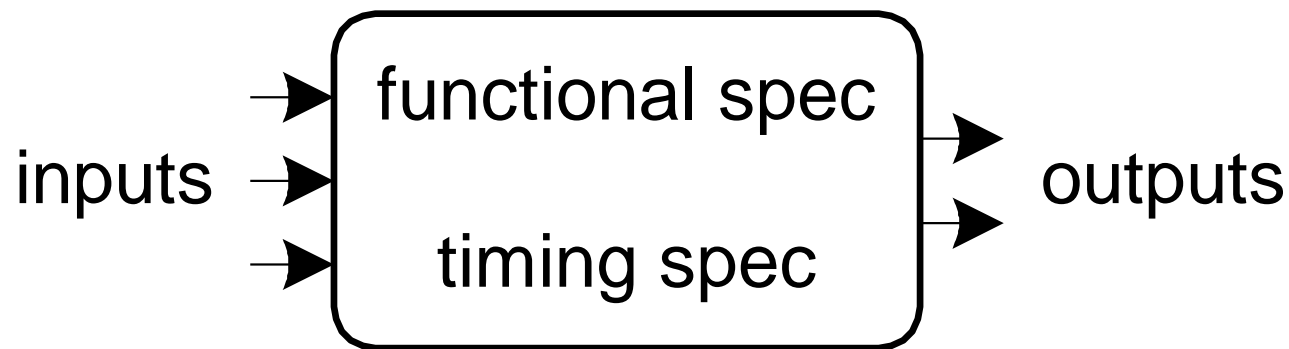- Inputs
- Outputs
- Functional specification
- Timing specification



Circuits

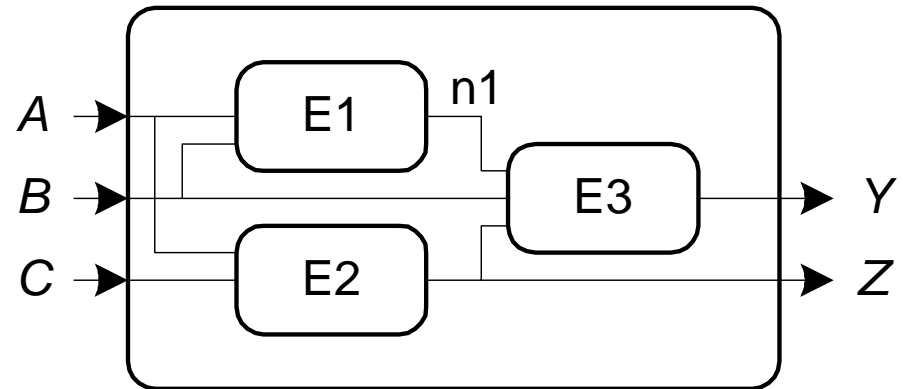- Nodes
 - Inputs: A, B, C
 - Outputs: Y, Z
 - Internal: $n1$
- Circuit elements
 - $E1, E2, E3$
 - Each a circuit



Types of Logic Circuits

- **Combinational Logic**


- Memoryless

- Outputs determined by current values of inputs

- **Sequential Logic**


- Has memory

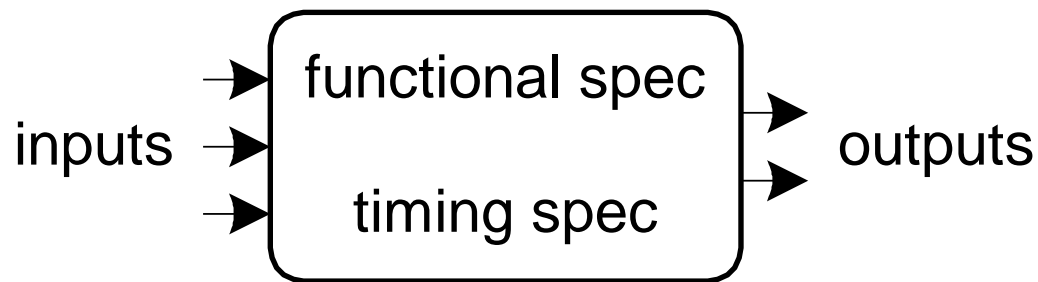- Outputs determined by previous and current values of inputs




Rules of Combinational Composition

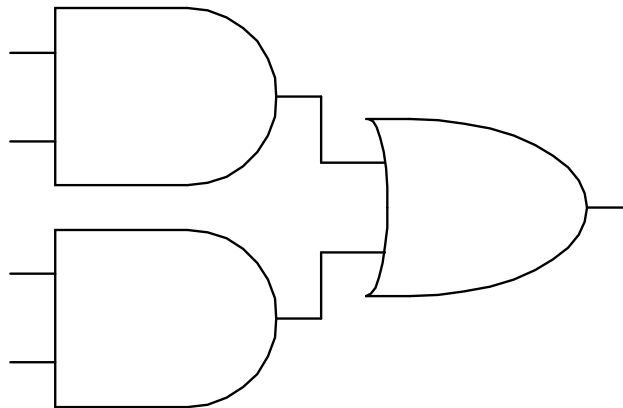- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
- **Example:**



Boolean Equations

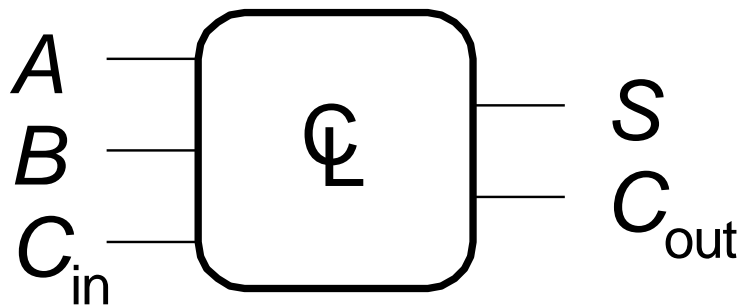- Functional specification of outputs in terms of inputs
- Example:** $S = F(A, B, C_{in})$
 $C_{out} = F(A, B, C_{in})$



$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

Some Definitions

- Complement: variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- Literal: variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- Implicant: product of literals
 $ABC, \bar{A}C, BC$
- Minterm: product that includes all input variables
 $ABC, \bar{A}\bar{B}\bar{C}, ABC$
- Maxterm: sum that includes all input variables
 $(A+\bar{B}+C), (\bar{A}+B+\bar{C}), (\bar{A}+\bar{B}+C)$



Sum-of-Products (SOP) Form

- All equations can be written in SOP canonical form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<i>A</i>	<i>B</i>	<i>Y</i>	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) =$$

Sum-of-Products (SOP) Form

- All equations can be written in SOP canonical form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) =$$

Sum-of-Products (SOP) Form

- All equations can be written in SOP canonical form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	m_0
0	1	1	$\bar{A} B$	m_1
1	0	0	$A \bar{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \bar{A}B + AB = \Sigma(m_1, m_3) = \Sigma(1, 3)$$

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS canonical form
- Each row has a **maxterm**
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- Form function by **ANDing** the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = F(A, B) = (A + B)(\overline{A} + B) = \Pi(M_0, M_2) = \Pi(0, 2)$$